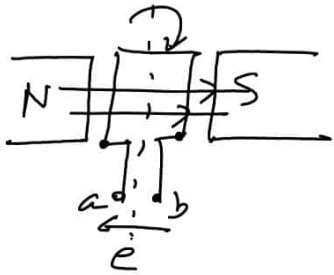





Lecture 11

28/12/2020

Single Phase System




\Rightarrow

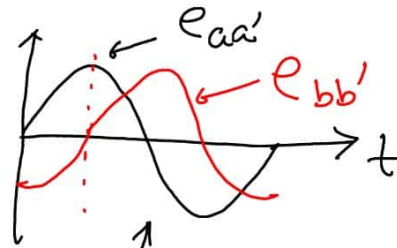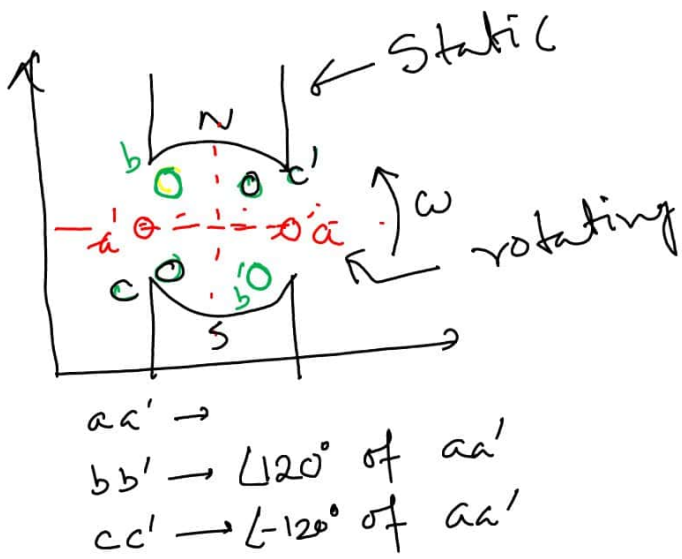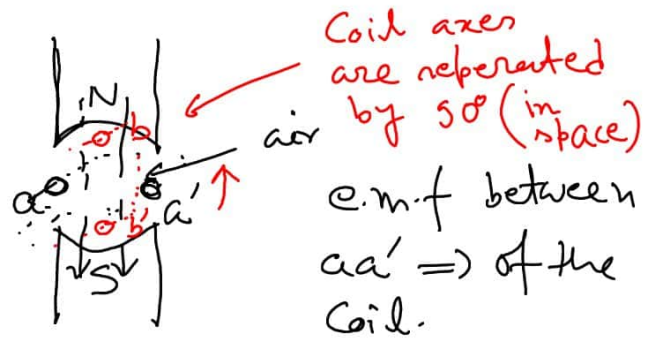

Two phase system


Voltages are phase separate by 90° .

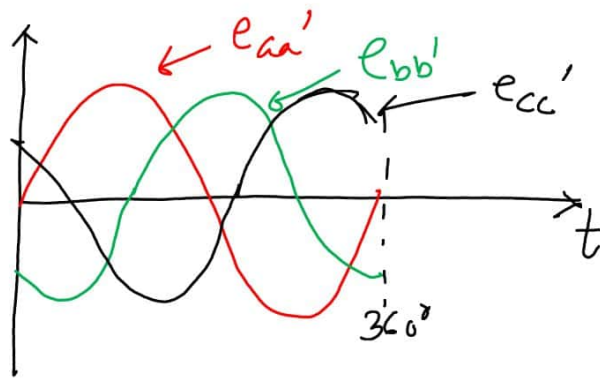

$\Rightarrow e_{aa'}, e_{bb'} \& e_{cc'}$
these voltage are
Phase separated by
 120° .

Synchronous Generator

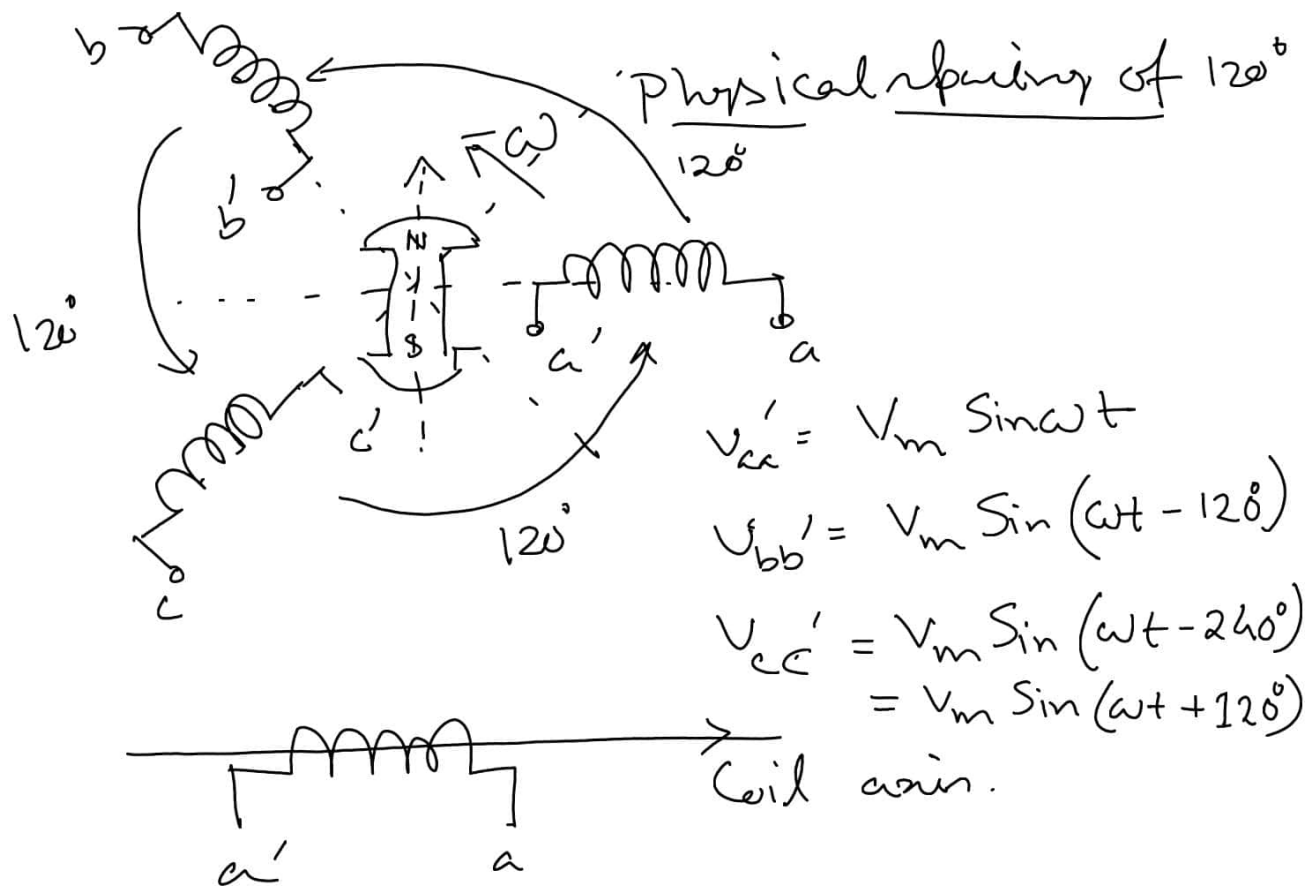\hookrightarrow This is used for electricity generation in thermal power plant, hydel power plants. Magnetic field line generation \Rightarrow is on the rotor 3 phase coils are on the stator.



3 ϕ System. \Rightarrow Balanced voltage generation.

$$V_{aa'} = V_m \sin \omega t$$

$$V_{bb'} = V_m \sin(\omega t - 120^\circ)$$

$$V_{cc'} = V_m \sin(\omega t + 120^\circ)$$

* Equal in magnitude
(Peak or RMS)

* Phase separated by 120° .

$$V_{aa'} + V_{bb'} + V_{cc'} = V_m \left[\sin \omega t + \sin(\omega t - 120^\circ) + \sin(\omega t + 120^\circ) \right]$$



$$= 0$$

$$\overline{V_{aa'}} = V \angle 0^\circ$$


$$\overline{V_{bb'}} = V \angle -120^\circ$$

$$\overline{V_{cc'}} = V \angle 120^\circ$$
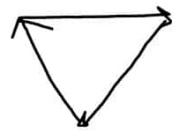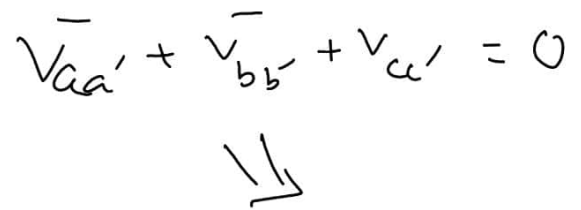
$$V = \frac{V_m}{\sqrt{2}} \Rightarrow \text{RMS value}$$



Equilateral

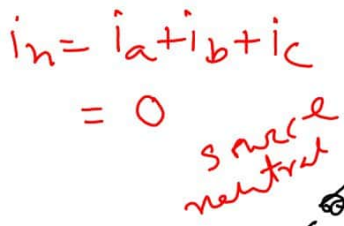

$$V_{an} = V_{a'a'} = V_m \sin \omega t \quad [Z \text{ impedance}]$$

$$V_{bn} = V_{b'b'} = V_m \sin(\omega t - 120^\circ) \quad "$$


$$V_{cn} = V_{c'c'} = V_m \sin(\omega t + 120^\circ) \quad "$$

$$\underline{Z = R + j\omega L} \quad (\text{Let } \text{var})$$

$$i_a = \frac{V_m}{|Z|} \sin(\omega t - \phi) \quad \phi = \tan^{-1} \frac{\omega L}{R}$$

$$i_b = \frac{V_m}{|Z|} \sin(\omega t - 120^\circ - \phi)$$

$$i_c = \frac{V_m}{|Z|} \sin(\omega t + 120^\circ - \phi)$$

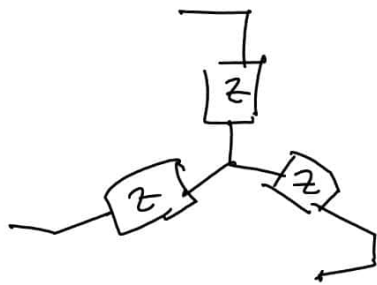


$\Rightarrow Z$ equal in all branches
(So balanced loading)

$\hat{i}_a, \hat{i}_b, \hat{i}_c$ are also balanced
3 ϕ currents.

\Rightarrow $\left\{ \begin{array}{l} \text{equal} \\ \text{magnitude} \\ \text{120}^\circ \text{ phase} \\ \text{separation} \end{array} \right.$

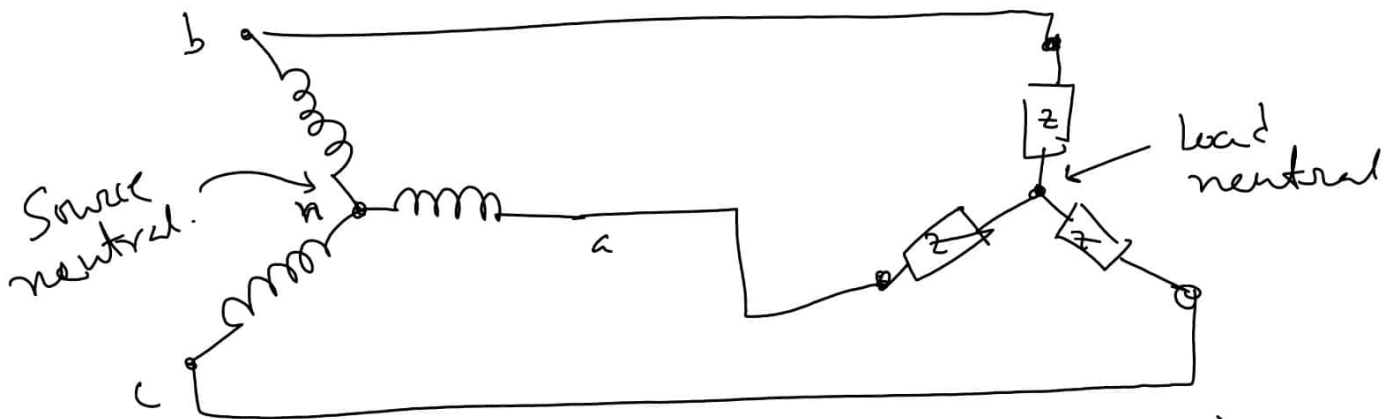
$$\text{So, } \hat{i}_a + \hat{i}_b + \hat{i}_c = 0$$




$3\phi - 3\text{Wire } (3\phi - 3W)$
Balanced System

Lecture-12
29/12/2020

Phasor diagram of Line and Phase voltage

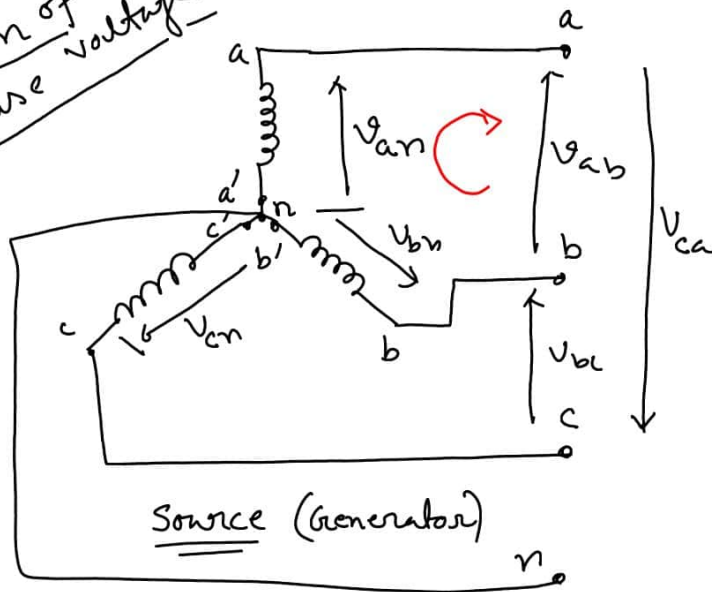

Star (1) Connected Source

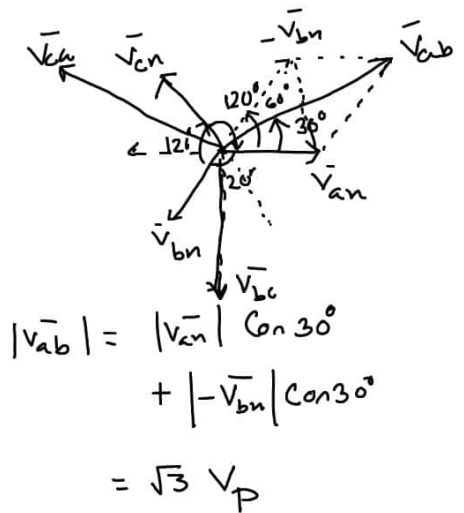

$V_{an}, V_{bn}, V_{cn} \Rightarrow$ Phase voltages.


$V_{ab}, V_{bc}, V_{ca} \Rightarrow$ Line voltages.

Phase voltage $\bar{V}_{an} = V_p \angle 0^\circ$; $\bar{V}_{bn} = V_p \angle -120^\circ$; $\bar{V}_{cn} = V_p \angle +120^\circ$

$\bar{V}_{ab} = \bar{V}_{an} - \bar{V}_{bn} = \sqrt{3} V_p \angle 30^\circ$ [referenced w.r.t. \bar{V}_{an}]

$$\bar{V}_{bc} = \bar{V}_{bn} - \bar{V}_{cn} = \sqrt{3}V_p \angle -90^\circ$$
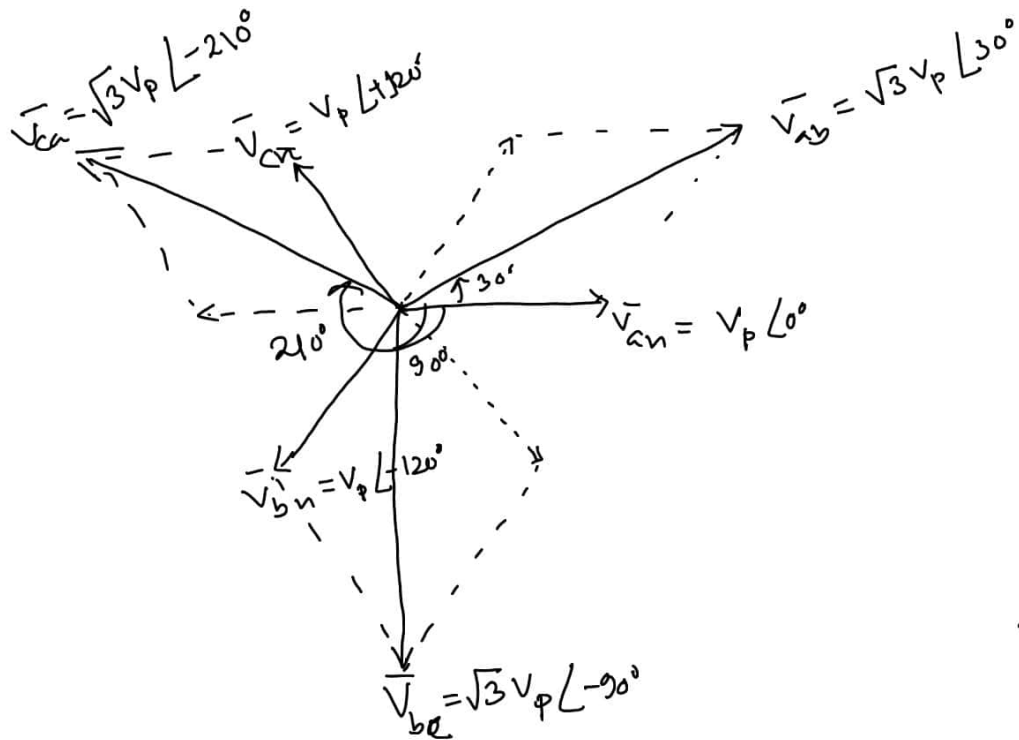
$$\bar{V}_{ca} = \bar{V}_{cn} - \bar{V}_{an} = \sqrt{3}V_p \angle -210^\circ$$



Phase voltage magnitude.

In the star connected system line voltage $|V_{LL}| = \sqrt{3} |V_p|$

Line voltages are also equal in magnitude & Phase separated by $120^\circ \Rightarrow$ A balanced system.

$$v_{an} = V_m \sin \omega t$$


$$v_{ab} = \sqrt{3} V_m \sin (\omega t + 30^\circ)$$

Phase lead of 30°
w.r.t. v_{an} .




$$V_{LL} = \sqrt{3} V_P$$

RMS RMS

3 ϕ 4 Wire system

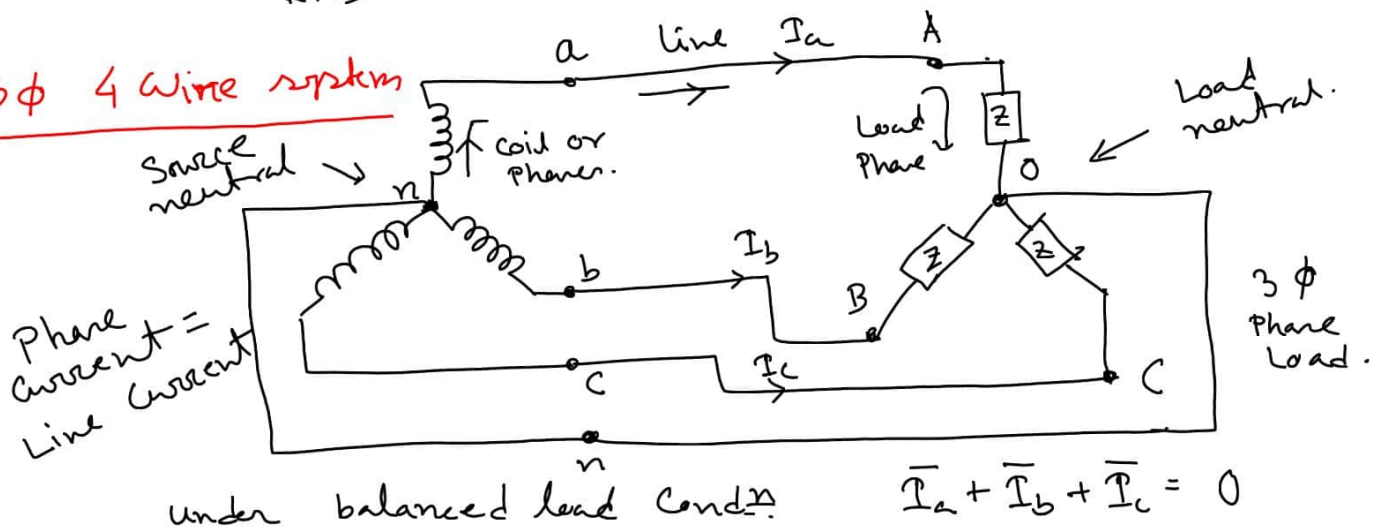

Delta Connected System

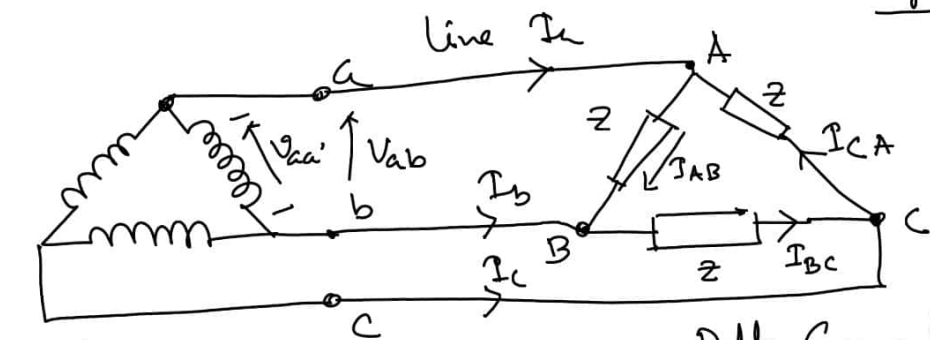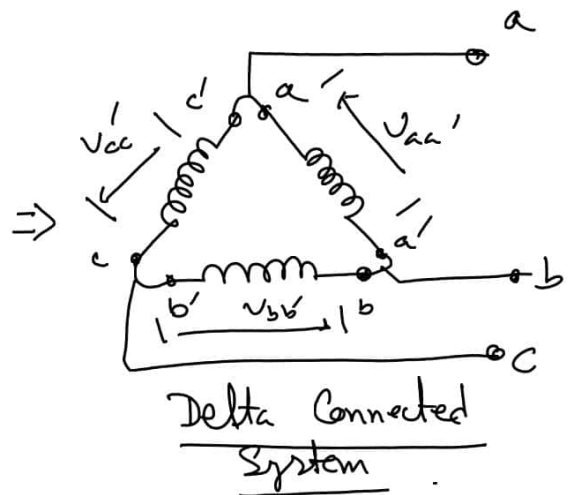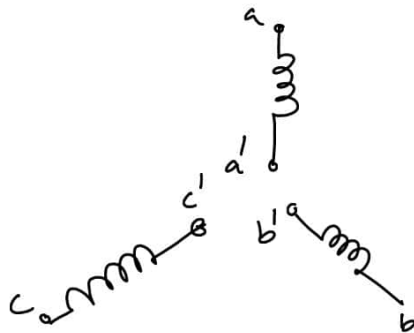

Delta Connected Source

Delta Connected load

$$\begin{aligned} \bar{I}_{AB} &= \frac{\bar{V}_{ab}}{Z} \\ \bar{I}_{BC} &= \frac{\bar{V}_{bc}}{Z} \\ \bar{I}_{CA} &= \frac{\bar{V}_{ca}}{Z} \end{aligned}$$

Phase Currents in Load.

Coil voltage = Phase voltage = Line voltage


Delta Connected system \Rightarrow Phase voltage = line voltage.

Line Currents.

$$\begin{cases} \bar{I}_A = \bar{I}_{AB} - \bar{I}_{CA} \\ \bar{I}_B = \bar{I}_{BC} - \bar{I}_{AB} \\ \bar{I}_C = \bar{I}_{CA} - \bar{I}_{BC} \end{cases}$$


$$|\bar{I}_{AB}| = |\bar{I}_{BC}| = |\bar{I}_{CA}| = I_P$$

Phase Current magnitude in load.

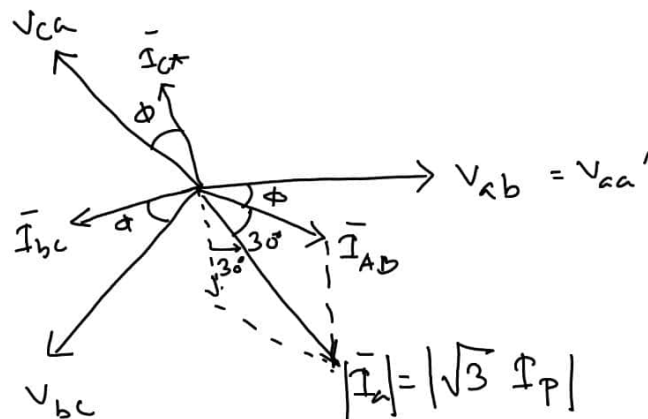

Line current = $\sqrt{3}$ x Phase current \Rightarrow Delta Connected System

Power

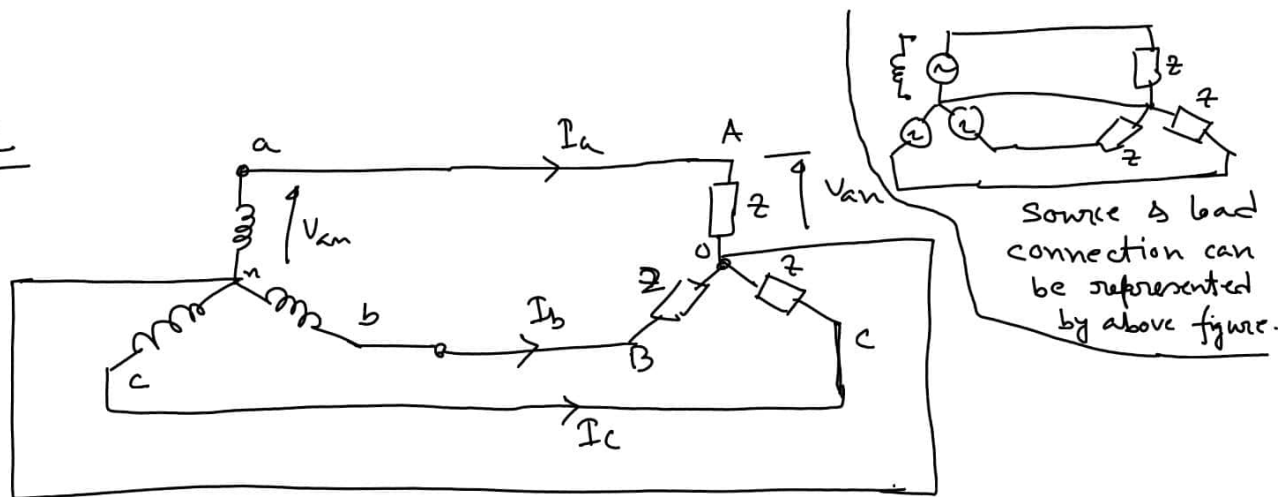

Power in Phase A $\rightarrow P_a = V_{an} \cdot i_a$

Instantaneous Power in the 3 phases —

$$V_{an} = V_m \sin \omega t$$

$$i_a = I_m \sin(\omega t - \phi)$$

$$I_m = \frac{V_m}{|Z|} ; \phi = \angle Z$$

$$\begin{aligned} p &= p_a + p_b + p_c \\ &= V_{an} i_a + V_{bn} i_b + V_{cn} i_c \\ &= 3 V_{ph} I_{ph} \cos \phi \end{aligned}$$

\nearrow RMS \searrow RMS

Average power $P = \frac{1}{2\pi} \int_0^{2\pi} p \, d(\omega t) = 3 V_{ph} I_{ph} \cos \phi$

Instantaneous power $p = v_{an} i_a + v_{bn} i_b + v_{cn} i_c$

$$= V_m I_m \sin(\omega t) \sin(\omega t - \phi) + V_m I_m \sin(\omega t - 120^\circ) \sin(\omega t - 120^\circ - \phi) + V_m I_m \sin(\omega t + 120^\circ) \sin(\omega t + 120^\circ - \phi)$$

$$V_m I_m \sin(\omega t) \sin(\omega t - \phi) = \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t - \phi)]$$

$$V_m I_m \sin(\omega t - 120^\circ) \sin(\omega t - 120^\circ - \phi) = \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t - 240^\circ - \phi)]$$

$$V_m I_m \sin(\omega t + 120^\circ) \sin(\omega t + 120^\circ - \phi) = \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t + 240^\circ - \phi)]$$

$$\therefore p = \frac{3}{2} V_m I_m \cos \phi - \underbrace{\frac{V_m I_m}{2} [\cos(2\omega t - \phi) + \cos(2\omega t - \phi - 120^\circ) + \cos(2\omega t - \phi + 120^\circ)]}_{=0}$$


$$\Rightarrow p = \frac{3}{2} V_m I_m \cos \phi = 3 \times \underbrace{V_{ph}} \times \underbrace{I_{ph}} \cos \phi \quad \begin{array}{l} \text{[Instantaneous power is} \\ \text{constant]} \end{array}$$

↑ ↑
RMS values.

Lecture - 13



01/01/2021

1.

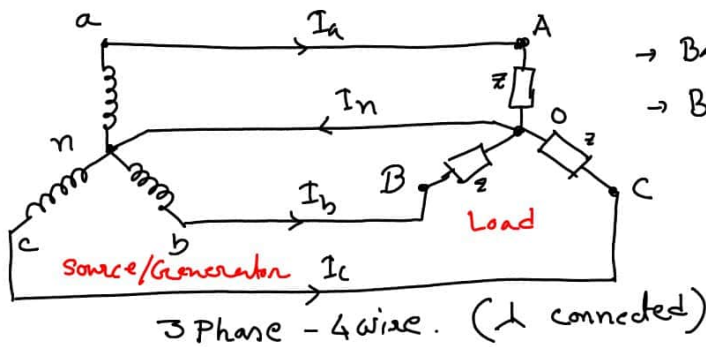

→ Balanced load
→ Balanced Source
 $I_a + I_b + I_c = I_n = 0$

2.

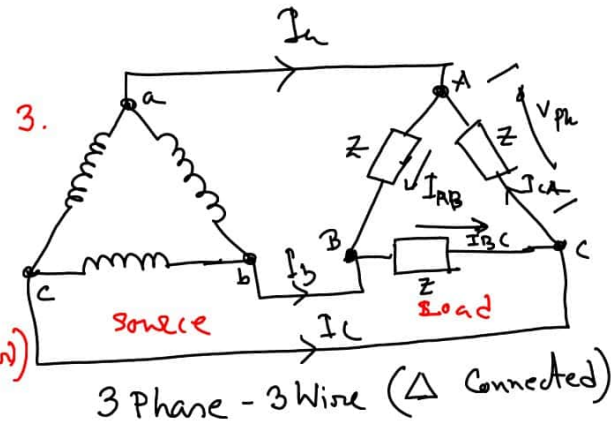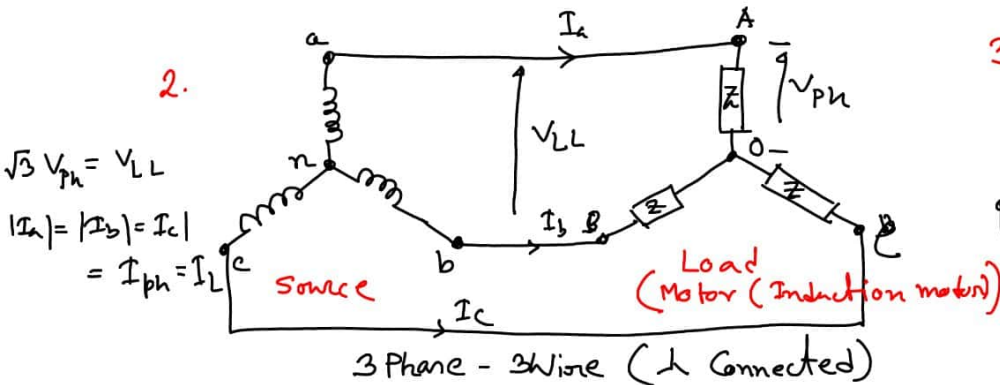

* Balanced load (for this course)

$$I_a + I_b + I_c = 0$$

Apply KCL

Phase current $\rightarrow |I_{AB}| = |I_{BC}| = |I_{CA}| = I_{ph}$

Line current $|I_a| = |I_b| = |I_c| = \sqrt{3} I_{ph} = I_L$

Active Power (Load consumes this to perform work)
active power = Average value of instantaneous power

$$P = 3 V_{ph} I_{ph} \cos \phi$$

Star Connected Load


$$\begin{aligned} P &= 3 V_{ph} I_{ph} \cos \phi \\ &= \sqrt{3} V_{LL} I_L \cos \phi \\ \left[V_{ph} &= \frac{V_{LL}}{\sqrt{3}} \right] \\ I_{ph} &= I_L \end{aligned}$$

Delta Connected Load

$$\begin{aligned} P &= 3 V_{ph} I_{ph} \cos \phi \\ &= \sqrt{3} V_{LL} I_L \cos \phi \\ \left[V_{ph} &= V_{LL} \right] \\ \left[I_{ph} &= \frac{I_L}{\sqrt{3}} \right] \end{aligned}$$

Apparent Power
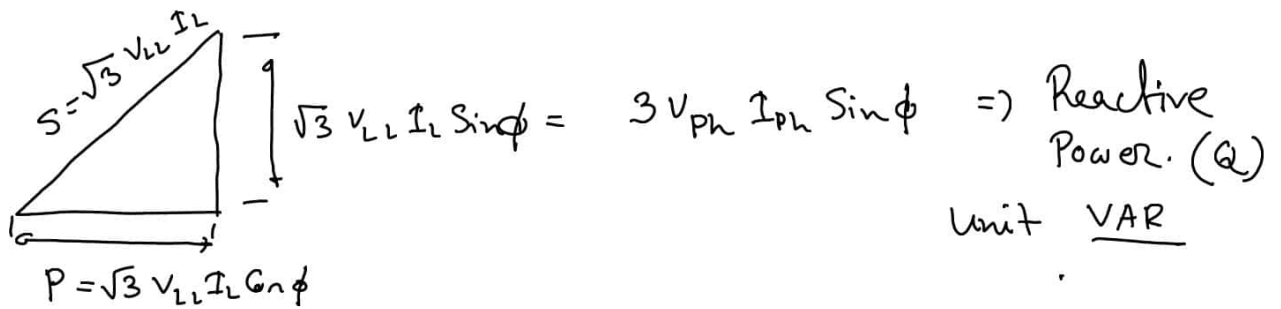
$$\begin{aligned} S &= 3 V_{ph} I_{ph} \quad (\text{unit in VA}) \\ &= \sqrt{3} V_{LL} I_L \end{aligned}$$



$$S = \sqrt{3} V_{LL} I_L$$

$$\sqrt{3} V_{LL} I_L \sin \phi = 3 V_{ph} I_{ph} \sin \phi \Rightarrow \text{Reactive Power (Q)} \text{ Unit VAR}$$

$$P = \sqrt{3} V_{LL} I_L \cos \phi$$

Complex Power

$$\bar{Z} = \frac{\bar{V}_{ph}}{\bar{I}_{ph}}$$

$$\text{or, } \bar{I}_{ph} = \frac{\bar{V}_{ph}}{\bar{Z}} = \left| \frac{V_{ph}}{Z} \right| \angle -\theta$$


$$\text{Individual Phases} \Rightarrow \text{Re} [3 \times \bar{V}_{ph} \times \bar{I}_{ph}^*] = \text{Active power } P \text{ (Watt)}$$

$$\hookrightarrow \text{Im} [3 \times \bar{V}_{ph} \times \bar{I}_{ph}^*] = \text{Reactive power } Q \text{ (VAR)}$$

$$\hookrightarrow \bar{V}_{ph} \times \bar{I}_{ph}^* = \text{Apparent power } S \text{ (VA)}$$

$$S = P + jQ$$

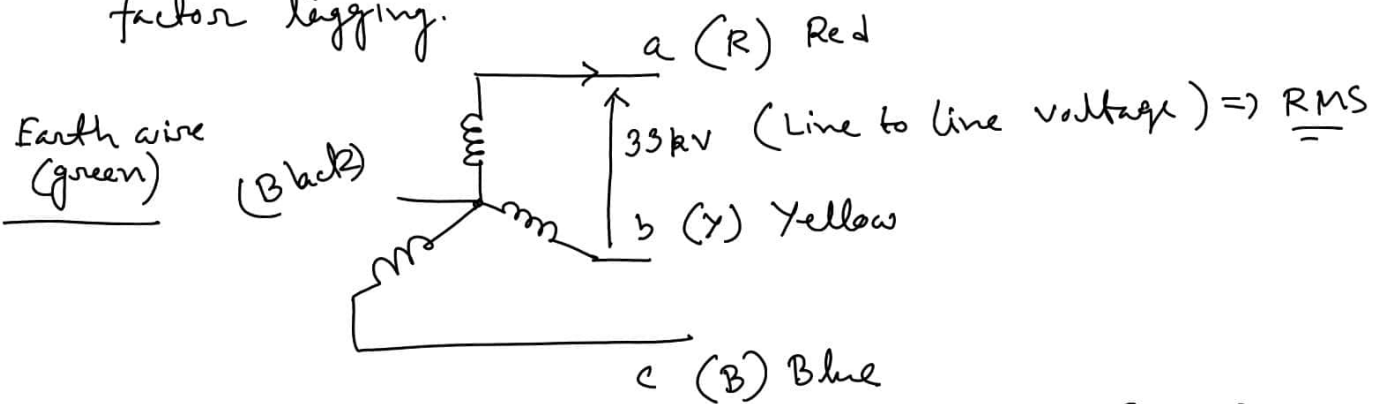* Calculate the line current of a connected 3 ϕ alternator delivering 5 MW at 33 kV and working at 0.8 power factor lagging.



$$|V_{ab}| = |V_{bc}| = |V_{ca}| = 33 \text{ kV (RMS)}$$

Line voltage $V_{LL} = 33 \times 10^3 \text{ V}$

Active Power $P = 5 \text{ MW} = 5 \times 10^6 \text{ W}$

power factor $\cos \phi = 0.8 \text{ (lagging)}$

$$\sqrt{3} V_{LL} I_L \cos \phi = P \quad \Rightarrow \quad I_L = \underline{\underline{109.4 \text{ A}}}$$

2. 3 ϕ Load. \Rightarrow 3 similar inductive coil ($R=50\Omega$; $L=0.3H$)

The supply is 3 ϕ , 415V & 50Hz.


- | | |
|---------------------|---|
| a) The line current | } i) star Connected
ii) delta Connected. |
| b) power factor | |
| c) The total power | |

* Supply is 3 ϕ , 415V, 50Hz

\hookrightarrow Balanced supply

$\hookrightarrow V_{LL} = 415V$.


$$Z = R + j2\pi fL = 50 + j94.2$$

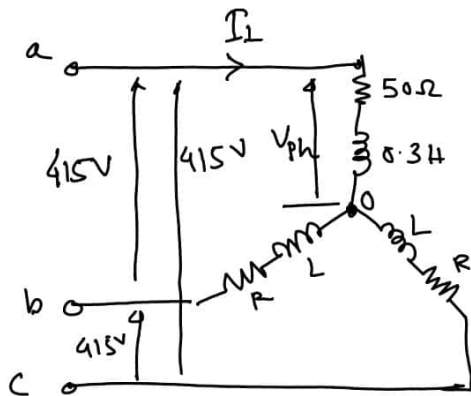

Balanced load.

$$\bar{I}_L = \bar{I}_{ph}$$

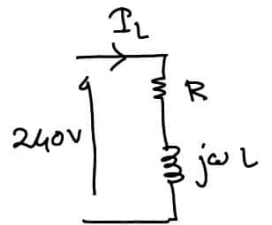
$$V_{ph} = \frac{V_{LL}}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 240V$$



$$\bar{I}_L = \frac{\bar{V}_{ph}}{R + j\omega L} = \frac{240 \angle 0^\circ}{50 + j94.2}$$

$$P = 3 V_{ph} I_{ph} \cos \phi = ? \quad \underline{\underline{\cos \phi = \frac{R}{|Z|}}}$$

b)

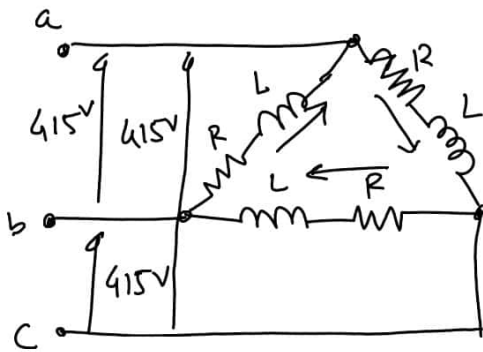

$$Z = R + j\omega L$$

$$|V_{LL}| = |V_{PW}| = 415$$

$$|I_{PW}| = \frac{415}{|R + j\omega L|}$$

Check the power consumed by the two loads.


Power Measurement

Wattmeter




Average value of power

Current Coil

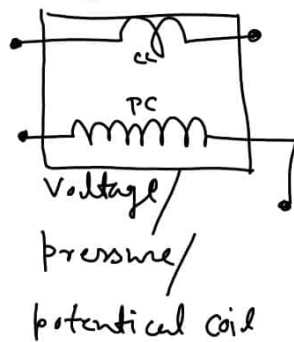

(very high impedance / Resistance)
almost zero current drawn by it

almost zero voltage drop in it.

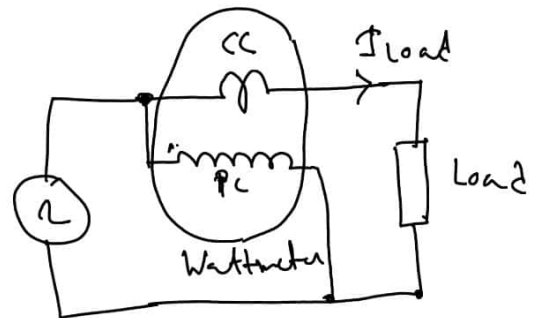


$$P = V I \cos \phi$$

\swarrow RMS \swarrow RMS \swarrow P.S.
 $\phi = \angle \frac{I}{V}$

Lecture-14

04/01/2021

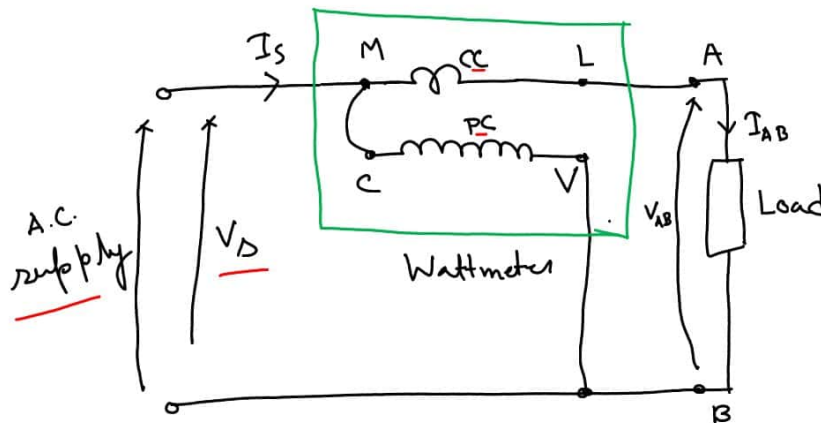

Wattmeter Connection

M \Rightarrow Mains ✓
 L \Rightarrow Load ✓
 C \Rightarrow Common ✓
 V \Rightarrow Voltage ✓

CC \Rightarrow Current coil
PC \Rightarrow Pressure coil/
 voltage coil

$$V_s \approx V_{AB} \quad (\text{negligible drop in 'cc'})$$

Wattmeter
 Reading \rightarrow Power
 (W)

$$P = \frac{|V_{AB}|}{I_{AB}} \times (\text{Cosine of angle bet}^n \text{ and})$$

RMS value of current through 'cc'


RMS value of voltage across 'PC'

voltage across 'PC'
 current through 'cc'

Measurement of three phase power

(Balanced system \rightarrow 3 phase 4 wire
 \rightarrow 3 phase 3 wire)

One Wattmeter Method :-


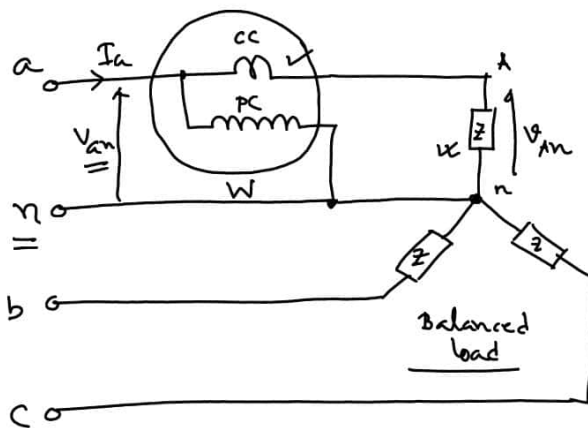


Total power = $3 \times$ power in one phase

* Neutral point is available for connection (3 ϕ 4 wire system)

Two Wattmeter Method

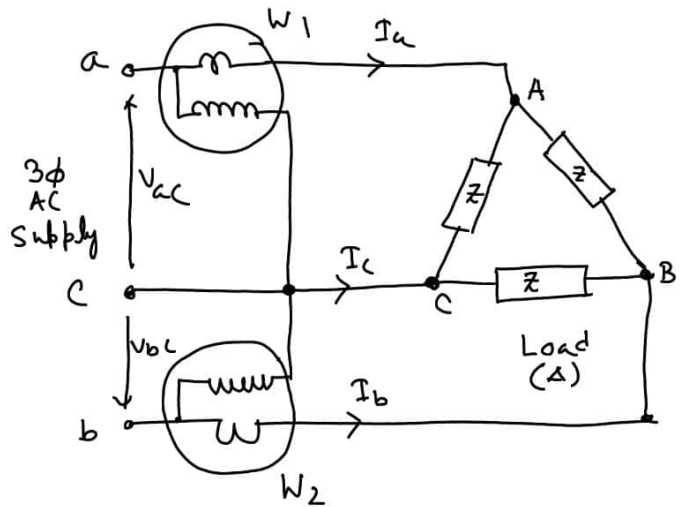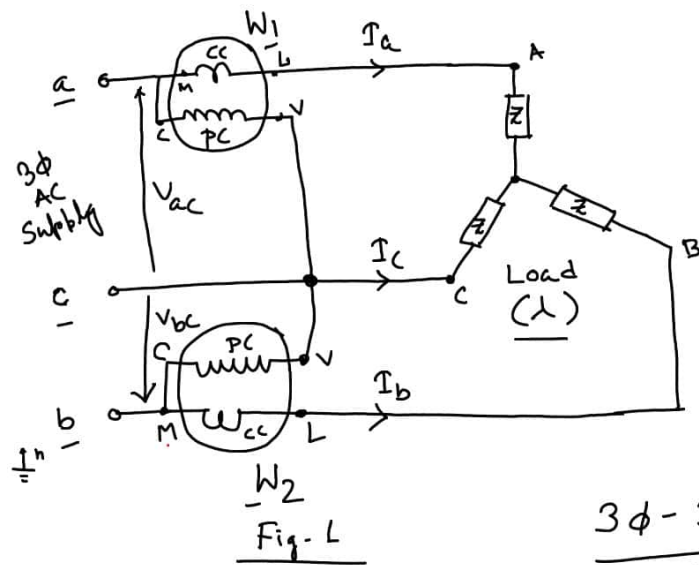\Rightarrow Phase relationship of supply phase voltage.



3 ϕ - 3 wire system (Balanced)


* Neutral point is not available.

Wattmeter $W_1 \rightarrow$
 $CC \rightarrow \underline{I_a}$ & $PC = \underline{V_{ac}}$ $\Rightarrow W_1 = |V_{ac}| |I_a| \cos(\angle_{V_{ac}}^{I_a})$

Wattmeter $W_2 \rightarrow$
 $CC \rightarrow \underline{I_b}$ & $PC = \underline{V_{bc}}$ $\Rightarrow W_2 = |V_{bc}| |I_b| \cos(\angle_{V_{bc}}^{I_b})$

Lagging load

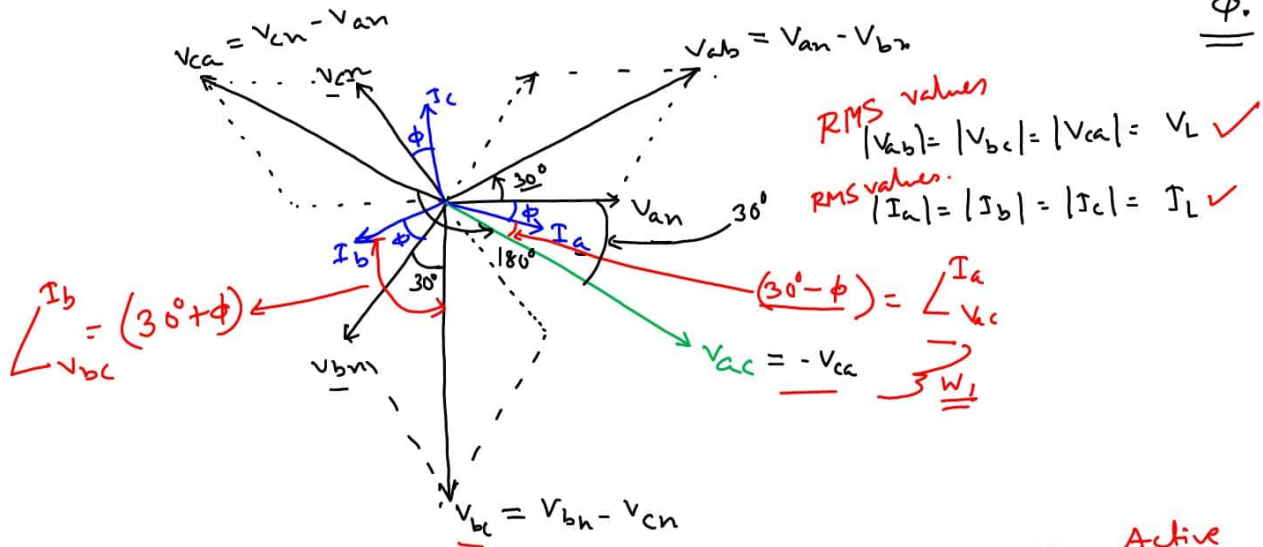Current I_a, I_b & I_c are lagging respective phase voltages by angle ϕ .



Reading of $W_1 \rightarrow$

$$W_1 = |V_{ac}| |I_a| \cos(30^\circ - \phi)$$

Reading of $W_2 \rightarrow$

$$W_2 = |V_{bc}| |I_b| \cos(30^\circ + \phi)$$

* Summation of $W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi = P(\text{Active Power})$

$$\therefore W_1 - W_2 = V_L I_L \cos(30^\circ - \phi) - V_L I_L \cos(30^\circ + \phi)$$

$$= V_L I_L \sin \phi = \frac{Q}{\sqrt{3}} = \frac{\text{Reactive Power}}{\sqrt{3}}$$

$$\therefore \sqrt{3} \frac{w_1 - w_2}{w_1 + w_2} = \tan \phi \quad \left| \therefore \phi = \tan^{-1} \left(\sqrt{3} \frac{w_1 - w_2}{w_1 + w_2} \right) \right.$$

↪ 45° angle. ✓

$\phi \Rightarrow$ Can vary from 0° to 90°

i) When $\phi = 0^\circ$ then $\cos \phi = 1$. (u.p.f.) unity power factor

$$\therefore W_1 = V_L I_L \cos(30^\circ - \phi) \Big|_{\phi=0^\circ} = \frac{\sqrt{3}}{2} V_L I_L$$

$$W_2 = V_L I_L \cos(30^\circ + \phi) \Big|_{\phi=0^\circ} = \frac{\sqrt{3}}{2} V_L I_L$$

Hence $W_1 = W_2$.

ii) When $0^\circ \leq \phi \leq 60^\circ$ i.e. $\cos \phi \text{ when } \phi = 0^\circ \rightarrow 1.0 \geq \cos \phi \geq 0.5 \Rightarrow$ W_1 & W_2 both are positive
and $W_1 > W_2$.

At $\phi = 60^\circ \Rightarrow$

$$W_1 = V_L I_L \cos(30^\circ - 60^\circ) = \frac{\sqrt{3}}{2} V_L I_L$$

$$W_2 = V_L I_L \cos(30^\circ + 60^\circ) = 0$$

So W_2 will read zero.
 $W = W_1 + W_2$

iii) When $60^\circ < \phi \leq 90^\circ$ i.e. $0.5 > \cos \phi \geq 0 \Rightarrow$ W_1 is positive but W_2 is negative.

* when W_2 reads negative then either 'pc' or 'cc' needs to be reversed and measurement of W_2 should be taken.

Then $W = W_1 + (-W_2) = W_1 - W_2$ (Calculation of Total power 'W' when W_2 is negative)


iv) At $\phi = 90^\circ$;

$$W_1 = 0.5 V_L I_L$$

$$W_2 = -0.5 V_L I_L$$

total power $W = W_1 + W_2 = 0$.

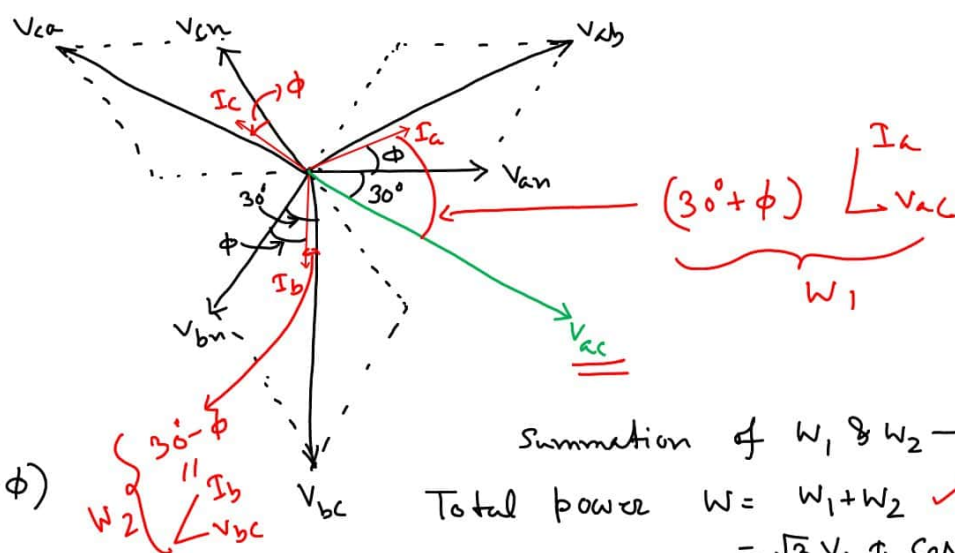Leading load
Capacitive load \Rightarrow Current is leading voltage



Reading of $W_1 \rightarrow$
 $W_1 = V_L I_L \cos(30^\circ + \phi)$

Reading of $W_2 \rightarrow$
 $W_2 = V_L I_L \cos(30^\circ - \phi)$

Summation of W_1 & $W_2 \rightarrow$
Total power $W = W_1 + W_2 \checkmark$
 $= \sqrt{3} V_L I_L \cos \phi \checkmark$

Calculation of $W_1 - W_2 = -V_L I_L \sin \phi$
 $\Rightarrow W_2 - W_1 = V_L I_L \sin \phi \leftarrow \frac{Q}{\sqrt{3}}$

* For leading power factor the readings of the Wattmeter are interchanged compared to the readings for lagging power factor.

	$\phi = 0^\circ$	$\phi = 30^\circ$	$\phi = 60^\circ$	$\phi = 90^\circ$	
$\cos(30^\circ + \phi)$	$\frac{\sqrt{3}}{2}$	$\frac{1}{2}$	0	$-\frac{1}{2}$	$\Rightarrow \cos(30^\circ - \phi) \geq \cos(30^\circ + \phi)$ $[0^\circ \leq \phi \leq 90^\circ]$
$\cos(30^\circ - \phi)$	$\frac{\sqrt{3}}{2}$	1	$\frac{\sqrt{3}}{2}$	$\frac{1}{2}$	

* $\tan \phi = \sqrt{3} \times \frac{\text{Greater Wattmeter Reading} - \text{Smaller Wattmeter reading}}{\text{Sum of Wattmeter reading}}$

Preferred Way:

1. Connect the Wattmeter with phase convention a,b,c (or R,Y,B) as shown in the connection diagram.
 (Phase convention wise $\rightarrow V_{an}$ is leading V_{bn} by 120° & V_{bn} is leading V_{cn} by 120° .)

2. Check the readings of wattmeters. If the readings are equal then its u.p.f.

If readings are unequal then mark ' W_1 ' to the wattmeter which is showing higher value. The other one as W_2 .

3. Reverse connection of W_2 if it is showing deflection in opposite direction. (Remember sign of W_2).

4. Now calculate $W = W_1 + W_2 = \text{Active power } P$

$$\text{and p.f. } \cos\phi = \cos\left[\tan^{-1}\left(\sqrt{3} \frac{W_1 - W_2}{W_1 + W_2}\right)\right]$$

lagging load
↓
Wattmeter 'cc' connected to phase a in W_1

leading load
↓
Wattmeter 'cc' connected to phase b is W_2

← leading or lagging from phase Convention & marking of W_1 & W_2 .

Reactive power $Q = \sqrt{3} (W_1 - W_2)$.

* 5.2 kW & 1.7 kW (motor load / lagging load). $V_L = 400 \text{ V}$.
 ↑ obtained after reversing the wattmeter connection.

a) Total power = ? ; b) p.f. = ? ; $I_L = ?$

a) $W = W_1 + W_2 = 5.2 + (-1.7) = 3.5 \text{ kW}$.

b) p.f. = $\cos\left(\tan^{-1}\left(\sqrt{3} \frac{W_1 - W_2}{W_1 + W_2}\right)\right) = 0.281$ lagging.

c) $I_L = \frac{P}{\sqrt{3} V_L \cos\phi} = \frac{3.5 \times 10^3}{\sqrt{3} \times 400 \times 0.281} = 17.98 \text{ A}$.