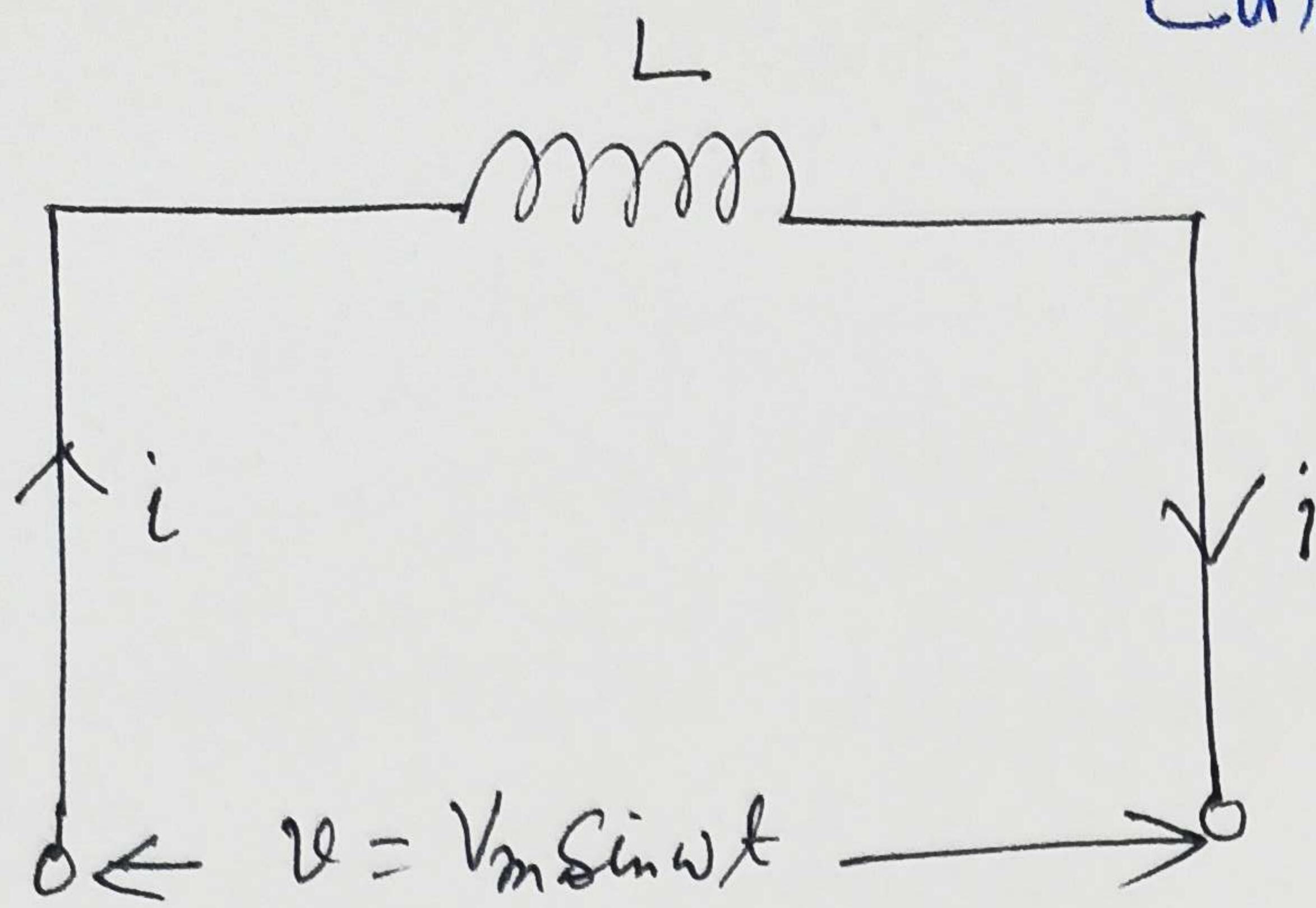


Current through a pure  
inductor. 1



$$e = -L \frac{di}{dt}$$

An applied voltage is equal and opposite to the self induced emf.

$$\text{Hence, } V = -e \\ = L \frac{di}{dt}$$

$$V = V_m \sin \omega t$$

$$L \frac{di}{dt} = V_m \sin \omega t$$

$$di = \frac{V_m}{L} \sin \omega t dt$$

~~Int~~ Integrating both sides of this equation.

$$\begin{aligned} i &= \int \frac{V_m}{L} \sin \omega t \cdot dt \\ &= \frac{V_m}{\omega L} (-\cos \omega t) \\ &= \frac{V_m}{\omega L} \sin \left( \omega t - \frac{\pi}{2} \right) \\ &= I_m \sin \left( \omega t - \frac{\pi}{2} \right) \end{aligned}$$

$$I_m = \frac{V_m}{\omega L}$$

The quantity  $\omega L$  is called the inductive reactance and is denoted by  $X_L$ .

### Power in purely inductive circuit

$$\begin{aligned} P &= V \times i \\ &= V_m \sin \omega t \times I_m \sin \left( \omega t - \frac{\pi}{2} \right) \end{aligned}$$

$$= -V_m I_m \sin \omega t \cos \omega t$$


$$= \frac{1}{2} V_m I_m \sin 2\omega t$$

$$\text{Average power for one complete cycle}$$

$$P = -\frac{1}{2} V_m I_m \text{ Average } (\sin 2\omega t) = 0$$

## A.C circuits containing Capacitance only

2

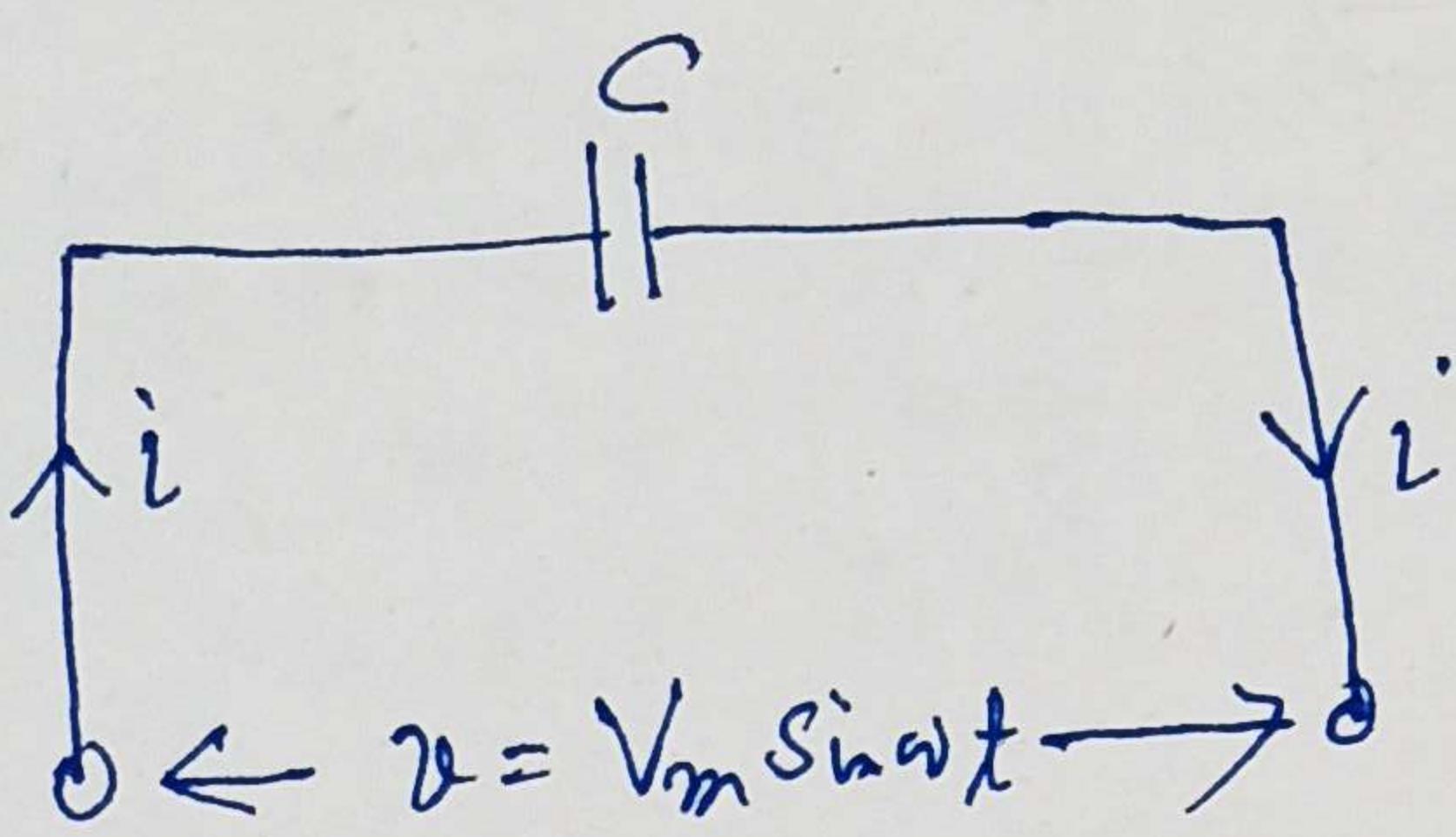

$i = C \times \text{Rate of change of potential difference}$

$$= C \frac{dV}{dt}$$

$$V = V_{\max} \sin \omega t$$

$$i = \frac{d}{dt} (V_m \sin \omega t)$$

$$= C \omega V_m \cos \omega t$$


$$= C \omega V_m \left( \sin \omega t + \frac{\pi}{2} \right)$$

$$= \frac{V_m}{\sqrt{C}} \sin (\omega t + \pi/2)$$

$$\text{The Max"} \text{ current } I_m = \frac{V_m}{\sqrt{C}}$$

$$\therefore i = I_m \sin (\omega t + \pi/2)$$

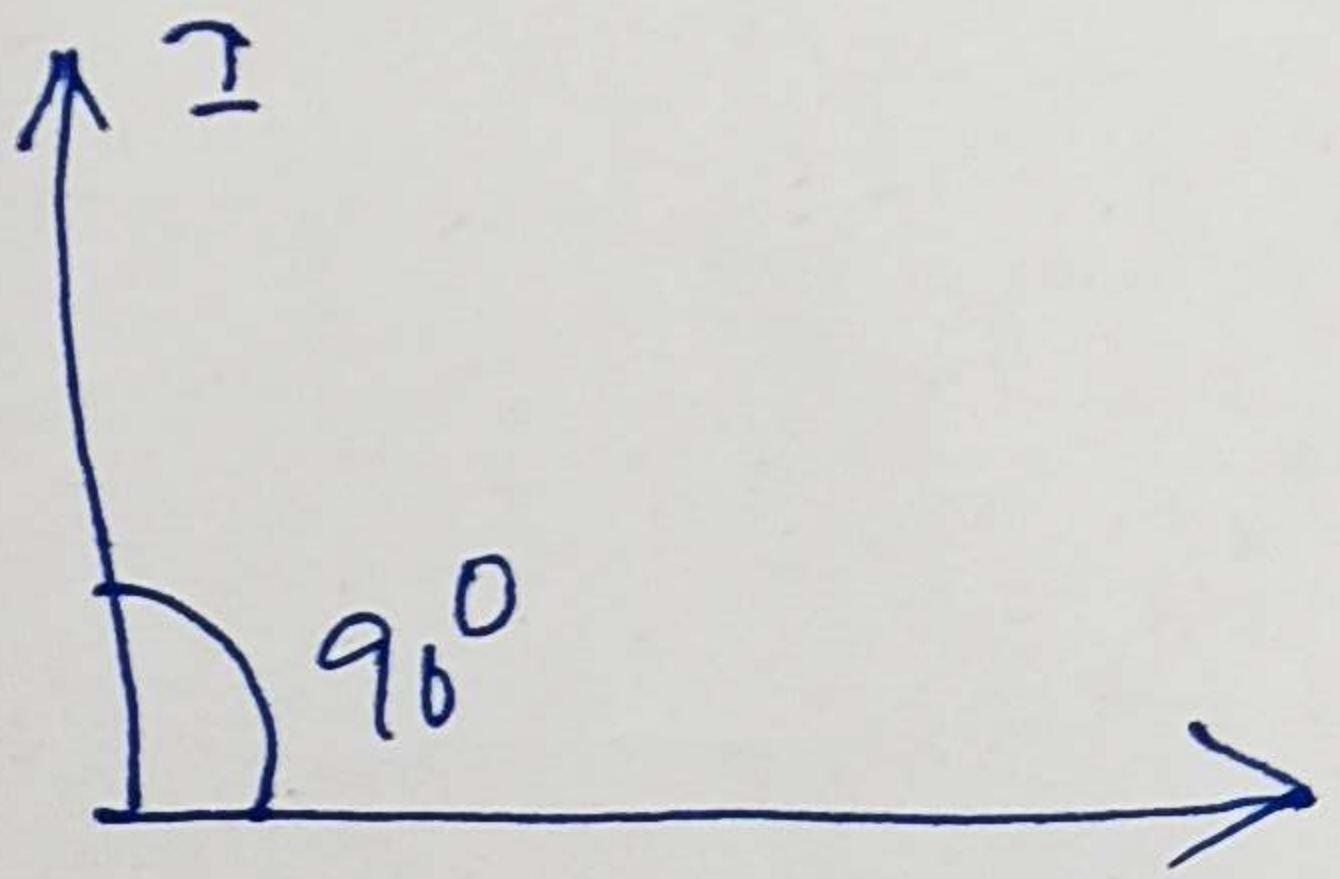The term  $\frac{1}{\sqrt{C}}$  is called the capacitive reactance and is denoted by  $X_C$ .



purely capacitive circuit

PMS in purely capacitive circuit

$$P = V \times i$$

$$= V_m \sin \omega t \times I_m \sin \left( \omega t + \frac{\pi}{2} \right)$$

$$= V_m \sin \omega t \cdot I_m \cos \omega t$$

$$= \frac{1}{2} V_m I_m \sin 2\omega t \quad \text{Average PMS for one complete cycle}$$

$$= \frac{1}{2} V_m I_m \times \text{Average of } (\sin 2\omega t) = 0$$

P1 A non inductive load takes 20A at 200 volts. Calculate the inductance of the reactor to be connected in series in order to the same current be supplied from 230 volts, 50Hz A.C supply. Also determine the power factor of the circuit.

Soln:-  $R = \frac{V_{r.m.s}}{I_{r.m.s}} = \frac{200}{20} = 10\Omega$

$$I_{r.m.s} = \frac{V_{r.m.s}}{Z}; \quad Z = \frac{230}{20} = \frac{23}{2}\Omega$$

$$X_L = \sqrt{Z^2 - R^2} \rightarrow L = 0.018 H.$$

$$P.f = \frac{\cos \phi}{\text{Power}} = \frac{R}{Z} = 0.8945 \text{ (lagging)}$$

P2 The voltage applied to a circuit:  $v = 100 \sin(\omega t + 30^\circ)$  and the current flowing in the circuit is:  $i = 15 \sin(\omega t + 60^\circ)$  Determine the impedance, resistance, reactance, power and power factor.

Soln:-  $V_{r.m.s} = \frac{100}{\sqrt{2}} V, \quad I_{r.m.s} = \frac{15}{\sqrt{2}} A$

$$Z = \frac{V_{r.m.s}}{I_{r.m.s}} = 6.666 \Omega$$

i Phase angle,  $\phi = 30^\circ$  (leading)

$$\text{Reactance}, X_C = Z \sin \phi = 3.333 \Omega$$

$$R = 5.773 \Omega, \quad P.f = \cos \phi = \cos 30^\circ = 0.866 \text{ (leading)}$$

$$\text{Power}, P = VI \cos \phi = 70.7 \times 10.6 \times 0.866 = 649 W.$$

P3 The current in a ~~series~~ circuit is given by  $(4.5 + j12)$ , when the applied voltage is  $(100 + j150) V$ . Determine ~~the~~: (i) Complex expression for the impedance 'i' (ii) Power and (iii) P.f.

Soln:-  $I = 12.816 \angle 69.44^\circ A,$

$$V = 180.27 \angle 56.30^\circ V$$

$$Z = \frac{V}{I} = \frac{180.27 \angle 56.30^\circ}{12.816 \angle 69.44^\circ} = 14.05 \angle -13.14^\circ \Omega$$

$\rightarrow$

$$= (13.68 - j3.19) \Omega \quad \text{capacitive}$$

(ii)  $P = VI \cos \phi = 180.27 \times 12.816 \times \cos(-13.14^\circ)$   
 $= 2.250 \text{ W}$

$\cdot \quad P_f = \text{Power factor} = \cos(-13.14^\circ) = 0.9738$

P4 A coil takes 2.5A, when connected across 200V, 50Hz main. The power consumed by the coil is found to be 400W. Find the inductance and power factor of the coil.

Soln: -  $P_{\text{max}} , \quad P = I^2 R = (2.5)^2 \times R = 400 \text{ W}$

~~$R = \frac{400}{6.25} = 64 \Omega$~~

$$\bar{Z} = \frac{V_{r.m.s}}{I_{r.m.s}} = \frac{200}{2.5} = 80 \Omega$$

$$X_L = 48 \Omega, \quad L = 0.153 \text{ H}$$

$$\cos \phi = \frac{R}{Z} = 0.8 \text{ (lagging)}$$

### Power in A.C. circuit

$$\begin{aligned} P &= V \times i \\ &= V_m \sin \omega t \times I_m \sin(\omega t - \phi) \\ &= \frac{1}{2} V_m I_m [\cos \phi - \cos(2\omega t - \phi)] \end{aligned}$$

$$= \frac{1}{2} V_m I_m \cos \phi - \frac{1}{2} V_m I_m \cos(2\omega t - \phi)$$

↓                      ↓  
 of remaining constant      average value

Average power in one cycle

$$P = V_{r.m.s} I_{r.m.s} \cos \phi \rightarrow \text{Active power}$$

$$\text{Apparent power} = V_{r.m.s} \times I_{r.m.s}$$

$$\begin{aligned} \text{Reactive power} \\ = V I \sin \phi \end{aligned}$$

Instantaneous values of voltage & current -

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \phi)$$

$\phi$  → phase angle by which current lags the voltage.

$V_m$ ,  $I_m$  are the peak values of voltage & current respectively.

$\omega$  = angular frequency ~~=~~ in rad/sec

$f$  = supply frequency in Hz.

$$\omega = 2\pi f.$$

$X$  → reactance in  $\Omega$ .


$Z$  → Impedance in  $\Omega$

$X_L$  → Inductive reactance in  $\Omega$

$X_C$  → Capacitive reactance in  $\Omega$

$$Z = R + jX \quad \text{in Complex form.}$$

$$|Z| = \sqrt{R^2 + X^2} \rightarrow \theta = \tan^{-1} \frac{X}{R}.$$

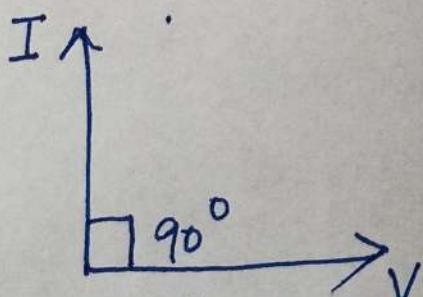

For purely ~~inductive~~ capacitive circuit

Problem:-

1. Find the current that will flow through a coil of negligible resistance and inductance of  $60\text{mH}$ , when connected to  $230\text{V}, 50\text{Hz}$  single phase supply. What will be the current if the frequency is (a) decreased to  $20\text{Hz}$  (b) increased to  $60\text{Hz}$ .

$$I = \frac{V}{X_L} = 12.2 \text{ A} = \frac{230}{18.86} \text{ Ans}$$

a)  $I = 30.49 \text{ A}$

→ All value are r.m.s.

b)  $I = 10.16 \text{ A}$


2. A capacitor of  $100\text{nF}$  is connected across a  $250\text{V}, 50\text{Hz}$  single phase supply. Calculate (i) the reactance of the capacitor (ii) r.m.s value of current (iii) maximum current.

i)  $X_C = \frac{1}{\omega C} = 31.8 \Omega$

ii)  $I_{\text{rms}} = \frac{V}{X_C} = 6.29 \text{ A}$  → R.M.S value of applied voltage

iii)  $I_{\text{max}} = I\sqrt{2} = 8.87 \text{ A}$

Series R-L circuit

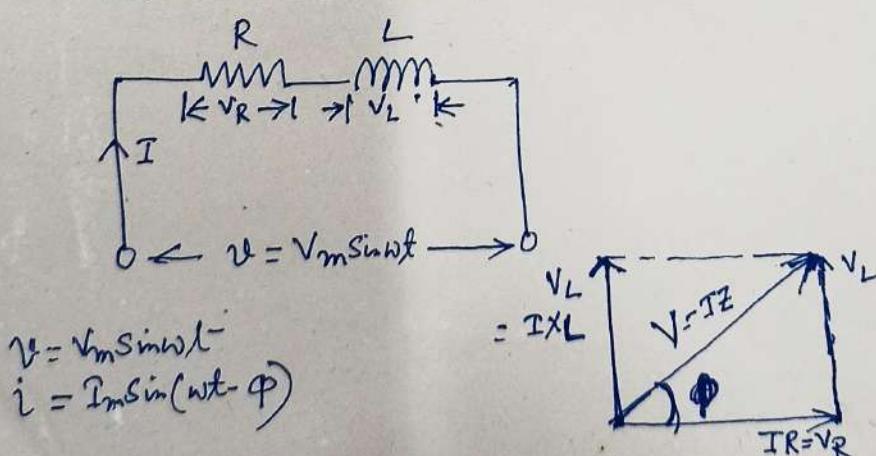


$$V = \sqrt{V_R^2 + V_L^2} = I \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$\tan \phi = \frac{IX_L}{IR} = \frac{X_L}{R} \rightarrow \phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{\omega L}{R}$$


FOR series RC circuit

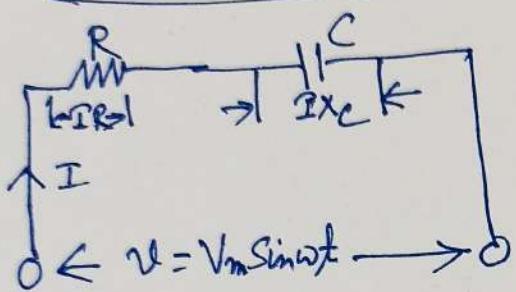

$$V = V_m \sin \omega t$$


$$I = I_m \sin(\omega t + \phi)$$
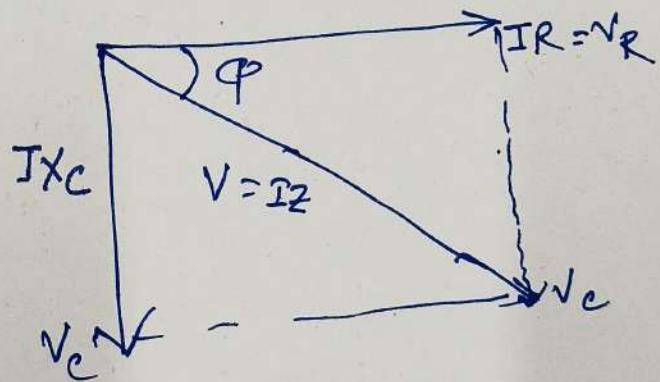
$$\phi = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \frac{1}{\omega C}$$



## Series R-L-C circuits

15.

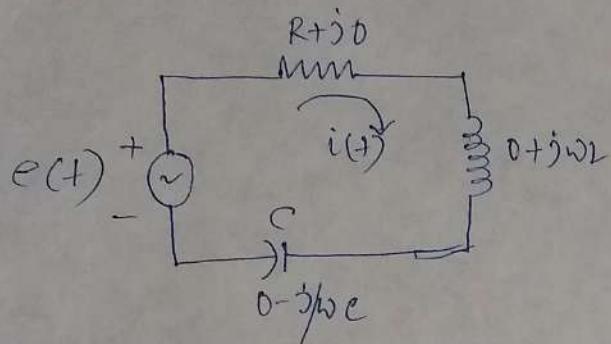

In this case, the total impedance is

$$\begin{aligned} Z_T &= (R + j\omega L) + \left(0 + j\omega L\right) \\ &\quad + \left(0 - j\frac{1}{\omega C}\right) . \end{aligned}$$


$$= R + j\left(\omega L - \frac{1}{\omega C}\right) \Omega$$

In terms of the magnitudes of the reactances, we have


$$Z_T = R + j(|X_L| - |X_C|) \Omega$$

$$|Z_T| = \sqrt{R^2 + (|X_L| - |X_C|)^2} \Omega , \quad \theta = \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$= \tan^{-1} \frac{|X_L| - |X_C|}{R}$$

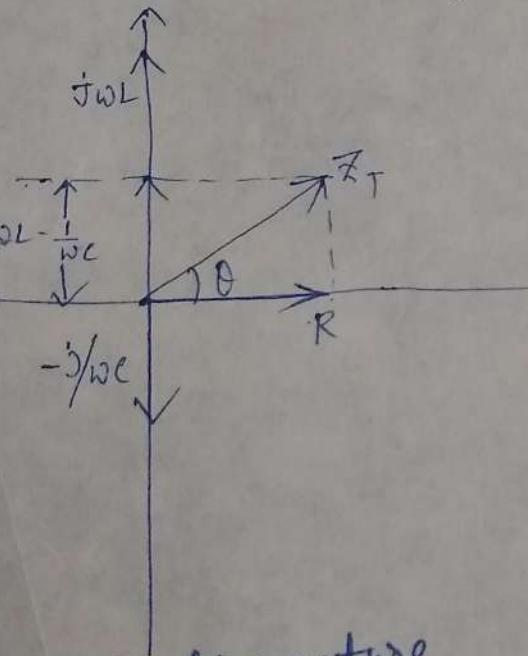

For inductive nature

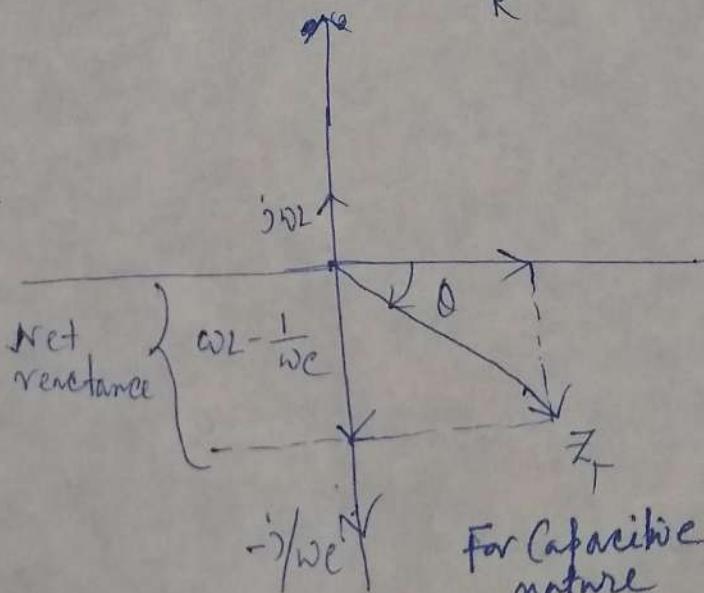

For capacitive nature

## Resonance in series R-L-C circuit - 2

For resonance,  $X_L = X_C$   
 ~~$\omega L = \frac{1}{\omega C}$~~

$$\boxed{Z = R}$$

Current becomes maximum at resonance condition.

Then at resonance, the frequency is called resonant frequency and determined from the relation,

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$\therefore f_r = \frac{1}{2\pi \sqrt{LC}}$$

We know,  $V_L = \text{voltage across inductor} = I \cancel{X_L}$

$$\begin{aligned} \text{At resonance, } V_L &= I \cdot 2\pi f_r L \\ &\geq I \cdot 2\pi \cdot \frac{1}{2\pi \sqrt{LC}} \cdot L \\ &= I \sqrt{\frac{L}{C}} \\ &= (V/R) \cdot \sqrt{\frac{L}{C}} = V \cdot \sqrt{\frac{L}{CR^2}} \end{aligned}$$

Voltage across a capacitor,

$$\begin{aligned} V_C &= I X_C = \cancel{I} \frac{1}{2\pi f_r C} \quad \text{at resonance} \\ &= \frac{V}{R} \left[ \frac{1}{\sqrt{C/L}} \right] = V \cdot \sqrt{\frac{L}{CR^2}} \end{aligned}$$

Again at resonance, voltage drop across the inductor and capacitor is equal in magnitude.

We see that at resonance, voltage magnification occurs during resonance.

Voltage magnification at resonance

$$= \frac{\text{Voltage across } L \text{ or } C}{\text{Supply voltage}}$$


$$= \frac{\sqrt{\frac{L}{CR^2}}}{\sqrt{}} = \sqrt{\frac{L}{CR^2}}$$

$$= \frac{\sqrt{L}}{R} \cdot \cancel{\frac{1}{\sqrt{C}}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{\sqrt{L}}{R} \cdot 2\pi f_r \cdot \sqrt{L} = \frac{\omega_r L}{L}$$

= This is called the Q factor

Q factor

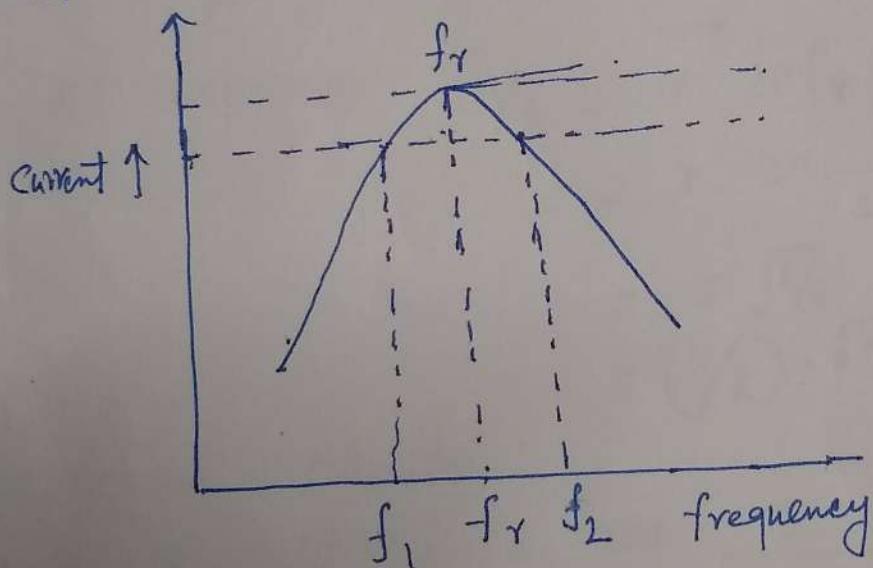

$f_1$  &  $f_2 \rightarrow$  half power frequency

$$I = \frac{V}{[R^2 + (\omega L - \frac{1}{\omega C})^2]^{\frac{1}{2}}} \cdot Y_2$$

at resonance,

$$I_m = \frac{V}{R} \text{ at resonance}$$

$$\text{Power at resonance, } I_m^2 R = \frac{V^2}{R^2} \cdot R$$

$$= \frac{V^2}{R} \text{ Watt.}$$

At resonance half force frequency,

$$\text{frequency} - \cancel{\text{current}} = \cancel{T_m}$$

Current becomes  $\frac{1}{\sqrt{2}}$  of current at resonance condition.

So forces at those frequencies become,

$$= \left( \frac{V}{\sqrt{2} R} \right)^2 \cdot R$$

$$= \frac{V^2}{2 R^2} \cdot R = \frac{V^2}{2 R} \text{ Watt}$$

$\Delta f = f_1 \sim f_2$  is the band width.

It can be shown,

$$\Delta f = f_1 \sim f_2 = \frac{R}{2 \pi L}$$

$$\text{Band width} = \Delta f = \frac{f_r R}{2 \pi f_r L}$$

$$\text{Again Q factor, } Q = \frac{2 \pi f_r L}{R}$$

$$\therefore \boxed{\Delta f = \frac{f_r}{Q}}$$

$$\text{Band width, } = \frac{\text{Resonant frequency}}{\text{Q factor.}}$$

5

1. A series R.L.C circuit is composed of a  $15\mu H$ ,  $10\Omega$  inductor and a  $10\text{PF}$  capacitor. Determine its band width.

Soln: -  $f_r = \frac{1}{2\pi\sqrt{LC}} = 4.11 \times 10^6 \text{ Hz}$

$$X_L = 2\pi f_r L = 387.2 \Omega$$

$$\Omega = \frac{X_L}{R} = \frac{387.2}{10} = 38.72$$

$$\text{Band width, } BW = \frac{f_r}{\Omega} = \frac{4.11 \times 10^6}{38.72} = 106.15 \mu\text{Hz}$$

2. A series LC circuit is resonance at  $150 \mu\text{Hz}$  and has a  $\Omega$  of 50. Find upper and lower cut off frequencies:-

$$BW = \frac{f_r}{\Omega} = \frac{150}{50} = 3 \mu\text{Hz}$$

upper half power frequency,

$$f_{upp} = \frac{BW}{2} + f_r = \frac{3}{2} + 150 = 151.5 \mu\text{Hz}$$

lower cut off freq,  $f_{low} = f_r - \frac{BW}{2} = 150 - \frac{3}{2} = 148.5 \mu\text{Hz}$

$\Omega$  factor

$\Omega$  factor of a series circuit indicates how many times the p.d across  $L$  or  $C$  is greater than the applied voltage at resonance. If  $\Omega$  factor is 20. and  $240\text{V}$  is the applied voltage across a series R-L-C circuit, then the voltage across the  $L$  or  $C$  at resonance is  $240 \times 20 = 480\text{V}$

Deduction of relation,

6

$$\Delta f = \frac{R}{2\pi L}$$

at half power frequency, i.e. at  $f_1$  or at  $f_2$

$$\frac{V}{\sqrt{2}R} = \frac{V}{[R^2 + (\omega L - \frac{1}{\omega C})^2]}^{1/2}$$

$$\therefore 2R^2 = R^2 + (\omega L - \frac{1}{\omega C})^2$$

$$\therefore R^2 = (\omega L - \frac{1}{\omega C})^2$$

$$\therefore \omega L - \frac{1}{\omega C} = \pm R$$

$$\therefore \omega^2 \pm \frac{R}{L}\omega - \frac{1}{LC} = 0$$

↓

$$\omega = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

for low values of  $R$ , the term,  $\frac{R^2}{4L^2}$  can be neglected.  
in comparison with the term  $\frac{1}{LC}$ .

$$\text{Then, } \omega = \pm \frac{R}{2L} \pm \sqrt{\frac{1}{LC}}$$

$$\text{Again, } \omega_r = \frac{1}{\sqrt{LC}}$$

$$\therefore \omega = \pm \frac{R}{2L} + \omega_r \quad \omega_r \text{ can be positive value only.}$$

$$\omega_1 = \omega_r + \frac{R}{2L}$$

$$\omega_2 = \omega_r - \frac{R}{2L}, \quad f_2 - f_1 = \frac{R}{2\pi L}$$

$$\therefore \omega_2 - \omega_1 = \frac{R}{L}$$

## Admittance and susceptance

The reciprocal of impedance is called admittance.

$$Y = \frac{1}{Z}$$

The terms "impedance" and "admittance" are quite descriptive: Impedance is a measure of the extent to which a component impedes the flow of ac current through it, while admittance is a measure of how well it admits the flow of current. The greater the impedance, the smaller the admittance and vice versa.

Conductance  $G = \frac{1}{R \angle 0^\circ} = \frac{1}{R} \angle 0^\circ$  Siemens Conductance is one form of admittance.

Reactance is another special case of impedance, so the reciprocal of reactance is a special case of admittance.

The reciprocal of reactance is ~~called~~ a special case of admittance. The reciprocal of reactance is called susceptance, denoted by  $B$ .


$$B = \frac{1}{X}$$

$$B_L = \frac{1}{X_L} = \frac{1}{\omega L \angle 90^\circ} = \frac{1}{\omega L} \angle -90^\circ \text{ Siemens}$$
$$= 0 - j(\frac{1}{\omega L}) \text{ Siemens.}$$

$$B_C = \frac{1}{X_C} = \frac{1}{(1/\omega C) \angle -90^\circ} = \omega C \angle 90^\circ \text{ Siemens.}$$

### Impedance triangle

For Inductive circuit -

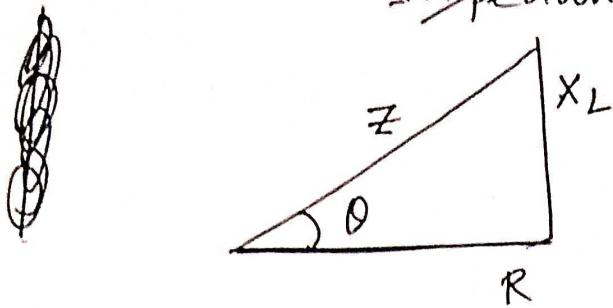

$$Z = \sqrt{R^2 + X_L^2}$$



$$G = Y \cos \theta$$

$$= Y \cdot \frac{R}{Z} = \frac{1}{Z} \cdot \frac{R}{Z}$$



$$= \frac{R}{Z^2}$$

$$B_L = Y \sin \theta$$

$$= \frac{1}{Z} \cdot \frac{X_L}{Z}$$

$$= \frac{X_L}{Z^2}$$

### For Capacitive circuit

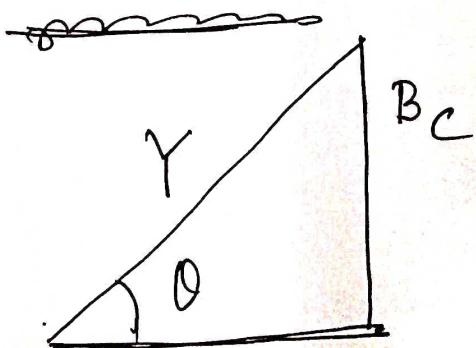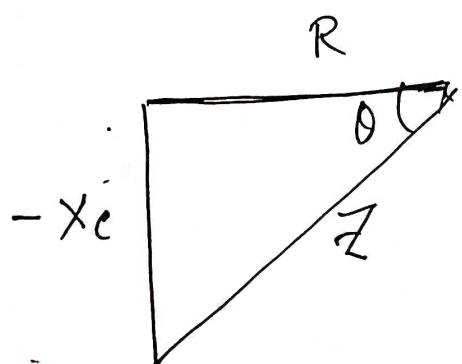

### Impedance triangle

$$Z = \sqrt{R^2 + X_C^2}$$

$$\tan \theta = \frac{B_C}{Z}$$

$$G = Y \cos \theta$$

$$= \frac{1}{Z} \cdot \frac{R}{Z} = \frac{R}{Z^2}$$

### Admittance triangle

$$B_C = Y \sin \theta$$

$$= \frac{1}{Z} \cdot \frac{X_C}{Z} = \frac{X_C}{Z^2}$$

P. A  $10\Omega$  resistor, a  $15.9\text{ mH}$  inductor and  $159\text{ }\mu\text{F}$  capacitor are connected in parallel to a  $200\text{ V}$ ,  $50\text{ Hz}$  source. Calculate the supply current and p.f.


$$X_L = 2\pi f L = 5\Omega$$

$$X_C = \frac{1}{2\pi f C} = 20\Omega$$

$$I_R = \frac{V}{R} = \frac{200}{10} = 20\text{ A} \text{ in phase with } V$$


$$I_L = \frac{V}{X_L} = \frac{200}{5} = 40\text{ A} \text{ lags } V \text{ by } 90^\circ$$

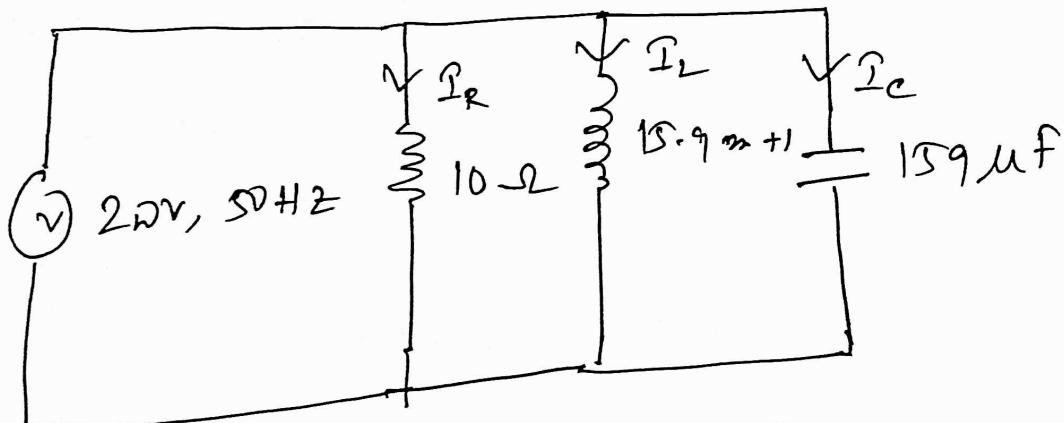
$$I_C = \frac{V}{X_C} = \frac{200}{20} = 10\text{ A} \text{ leads } V \text{ by } 90^\circ$$



$$I = \sqrt{I_R^2 + (I_L - I_C)^2} = 36\text{ A}$$
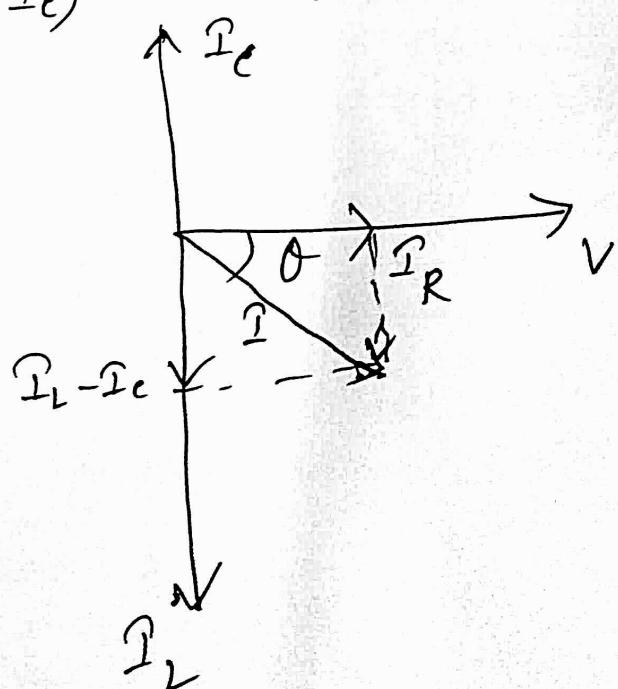
$$\cos \phi = \frac{I_R}{I} = \frac{20}{36} = 0.56 \text{ lag}$$



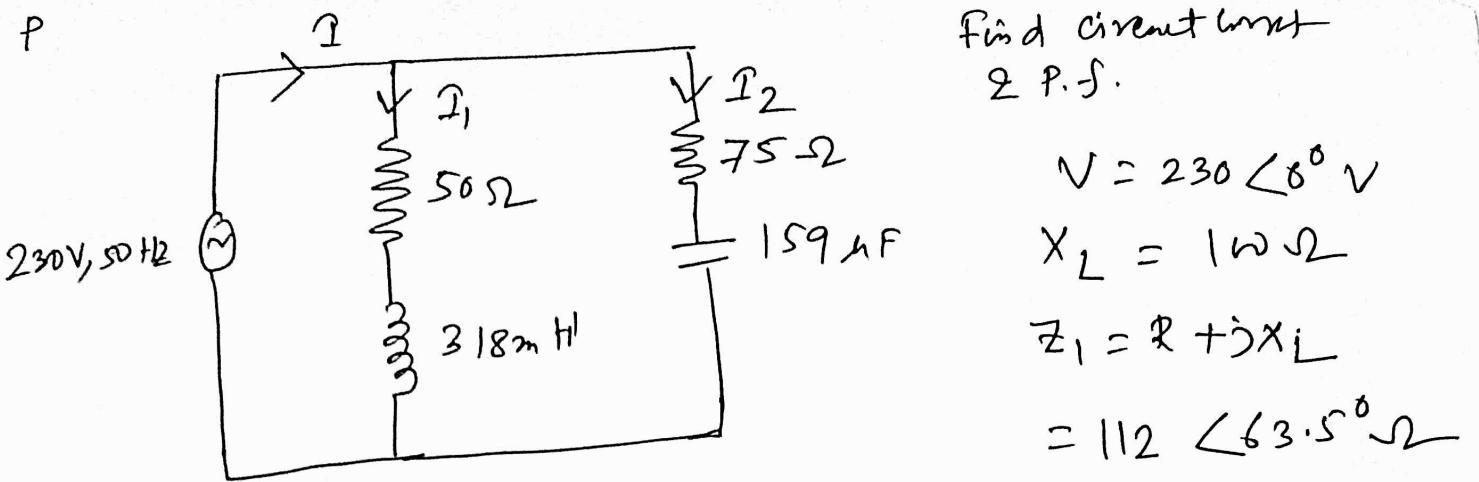

$$I_1 = \frac{V}{Z_1} = 0.91 - j1.83 A$$

$$X_C = 20 \Omega, \quad Z_2 = R_2 - jX_C \\ = 77.6 \angle -15^\circ \Omega$$

$$I_2 = \frac{V}{Z_2} = 2.96 \angle 15^\circ A \\ = (2.86 + j0.766 A)$$

Supply current,  $I = I_1 + I_2 = 3.92 \angle -15.7^\circ A$

$\text{BSCP} = 0.963 \log$