

Name:

ADM No:

Section:


SEMESTER: MONSOON, SESSION: 2022-2023

Subject: Basics of Electronics Engineering [Quiz-1]
Time: 40 Mins

Subject Code: ECI101
Maximum Marks: 26

Instructions: **Tick only the correct option. Each Question carries 2 marks.**

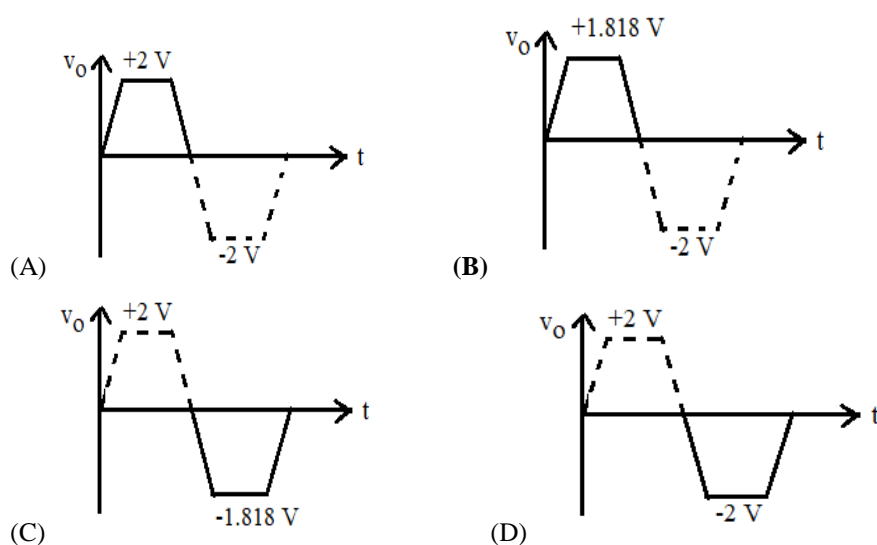1. The forward bias voltage required by a pn-junction diode with saturation current 10^{-2} nA to produce a current of $150 \mu\text{A}$ is [$V_T = 26 \text{ mV}$]
(A) 0.34 V (B) **0.43 V** (C) 0.7 V (D) 0 V
2. Consider a pn-junction diode biased at $I_{DQ} = 1 \text{ mA}$. A sinusoidal voltage is superimposed on V_{DQ} such that peak-to-peak sinusoidal current is $0.05 I_{DQ}$. The value of the applied peak-to-peak sinusoidal voltage is [$V_T = 26 \text{ mV}$]
(A) 701.3 mV (B) 700 mV (C) 26 mV (D) **1.3 mV**
3. In the voltage regulator circuit given in **Fig. 1**, the Zener diode current is to be limited to the range **5 mA to 100 mA**. The possible load resistances are
(A) **40 Ω to 192 Ω** (B) 21.33 Ω to 160 Ω (C) 40 Ω to 160 Ω (D) 21.33 Ω to 192 Ω
4. In the following voltage regulator circuit shown in **Fig. 2**, the maximum Zener power is **400 mW**. The current through the Zener diode is
(A) 45 mA (B) 26.3 mA (C) **18.7 mA** (D) 40 mA
5. The input voltage to a half-wave rectifier (diode is forward biased at positive half-cycle) is a triangular wave with **20 V** peak-to-peak with zero time-average value. The diode has a knee voltage of **0.6 V** and forward resistance of **20 Ω** . Assuming piecewise linear diode model, the peak output voltage can be found as
(A) **9.22 V** (B) 10.6 V (C) 18.4 V (D) 9.4 V
6. Consider the diode clipper circuit shown in **Fig. 3**. Assuming the diode is ideal, the output waveform will look like,



7. In **Fig. 4**, consider the input wave applied to the circuit is a square wave with **8 V** peak-to-peak with zero time-average value. The output waveform will be a square wave between

- (A) -2 V and +6 V (B) +2 V and +10 V (C) -2 V and -10 V (D) +2 V and -6 V
8. Identify the region of operation for the circuit given in **Fig. 5**. Assume β is very high i.e. $I_B=0$. Given $R_1 = 4.7 \text{ k}\Omega$ and $R_2 = 3.3 \text{ k}\Omega$.
(A) Active Region (B) Cut-off Region (C) Saturation Region (D) Reverse Active Region
9. Consider the circuit given in **Fig. 6**. Find out the V_{B2} . Take $V_{BE1} = V_{BE2} = 0.7 \text{ V}$ and $\beta_1 = \beta_2 = 100$.
 (A) 0.5 V (B) 0.6 V (C) 1.0 V **(D) 1.1 V**
10. For the transistor shown in **Fig. 7**, $\beta = 50$ The value of voltage V_{EC} is:
 (A) 3.13 V (B) 4.24 V (C) 5.18 V **(D) 6.07 V**
11. The JFET in the circuit shown in **Fig. 8** has an $I_{DSS} = 10 \text{ mA}$ and pinch-off voltage, $V_P = -5 \text{ V}$. The value of resistance, R_S for the drain current, $I_{DS} = 6.4 \text{ mA}$ is?
 (A) 0.82 $\text{k}\Omega$ (B) 0.24 $\text{k}\Omega$ **(C) 0.16 $\text{k}\Omega$** (D) 0.32 $\text{k}\Omega$
12. The circuit given below in **Fig. 9** is of the N-Channel JFET. The pinch-off voltage V_P and maximum saturation current, I_{DSS} are -8 V and 10 mA respectively. Calculate the drain current I_D ?
 (A) 25 mA **(B) 2.5 mA** (C) 30 mA (D) 3.0 mA
13. For the circuit given below in **Fig. 10**, Find the voltage at the emitter terminal (V_E) and emitter current (I_E). Assume $V_{BE} = 0.7 \text{ V}$, $\beta = 100$.
 (A) 4.3 V, 1.33 mA (B) 3.87 V, 1.33 mA (C) 4.3 V, 1.29 mA **(D) 3.87 V, 1.29 mA**

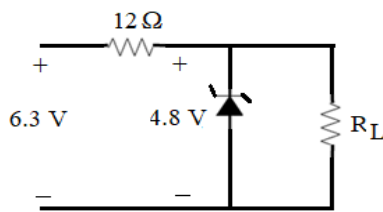


Fig. 1

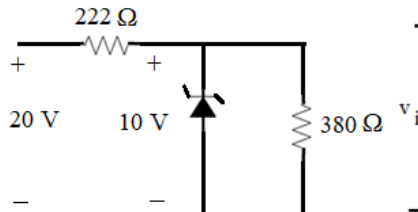


Fig. 2

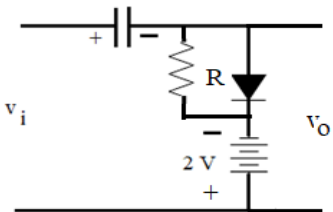


Fig. 4

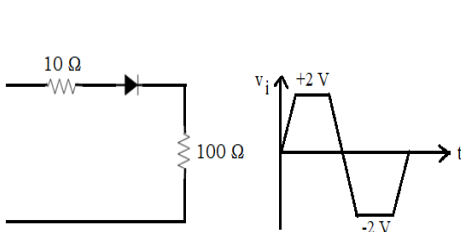


Fig. 3

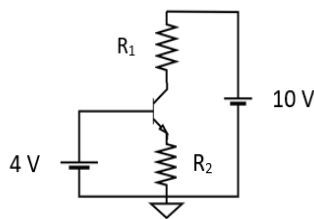


Fig. 5

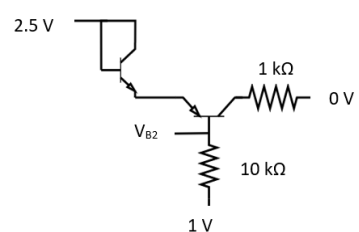


Fig. 6

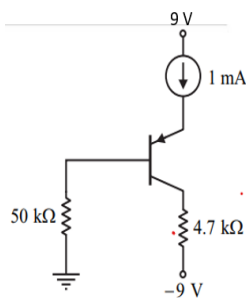


Fig. 7

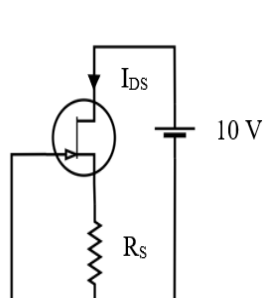


Fig. 8

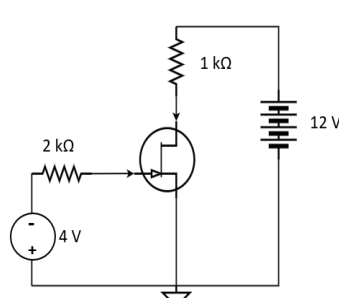


Fig. 9

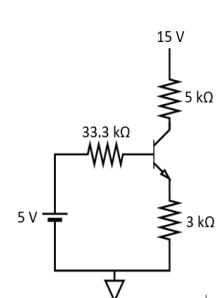


Fig. 10