

Name of the Student	Admn. Number	Signature
---------------------	--------------	-----------

Section-I – Answer all Questions (1 Mark Each)

- Q1.** In Thevenin's theorem, the Thevenin's equivalent voltage is computed by, **[1M]**
- a) **Measuring voltage across load terminals when load is open circuited**
 b) Measuring voltage across load terminals when load is short circuited
 c) Measuring voltage across the load when the load is connected
 d) Neglecting the independent energy sources.

- Q2.** Source transformation is applicable to both ideal as well as practical voltage and/or current sources. **[1M]**
- a) True **b) False**

- Q3.** A parallel AC circuit in resonance will: **[1M]**
- a) Have a high voltage developed across inductive and capacitive section
b) Have a maximum magnitude of impedance
 c) Have a maximum magnitude of admittance
 d) Act either like an inductor of high value or a capacitor of low value

- Q4.** In any network, the efficiency of the power, transferred to the load resistance, can be made maximum if the Thevenin's equivalent resistance across the load terminals is made: **[1M]**
- a) **Much smaller than the load resistance**
 b) Much larger than the load resistance
 c) Equal to the load resistance d) Five times the load resistance.

- Q5.** In a single-phase AC circuit having series-connected R, L, and C branches, the magnitude of voltage across resistor, inductor and capacitor are 30 V, 60 V and 20 V respectively. The magnitude of applied voltage is _____. **[1M]**
- a) 30V **b) 50 V** c) 70 V d) 90 V

- Q6.** A voltage $v(t) = 230\sqrt{2}\sin(2\pi 50t - 20^\circ) V$ is applied to a series RLC circuit, with $R = 2.5 \Omega$, $L = 60 \text{ mH}$, and $C = 6.8 \mu\text{F}$. If voltage phasor is taken as reference, the current phasor with respect to the voltage, is approximately, **[1M]**
- a) **0.512 $\angle -89.7^\circ$ A (I leads V by 89.7°)** b) $0.724 \angle -89.7^\circ$ A
 c) $0.724 \angle -109.7^\circ$ A d) $1.023 \angle -89.7^\circ$ A


- Q7.** The current (i) flowing through 5Ω resistor of the following circuit, due to 10 V source alone, is, **[1M]**

a) **0.4 A**

b) 0.5 A

c) 10/21 A

d) 10/31 A

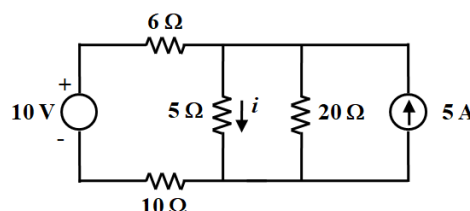


- Q8.** A current phasor of $(120 - j50) A$ flows through a circuit when the applied voltage phasor is $(8 + j12) V$. The complex power is: **[1M]**
- a) **$360 + j1840 \text{ VA}$** ; b) $1560 + j1040 \text{ VA}$; c) $360 - j1840 \text{ VA}$; d) $1560 - j1040 \text{ VA}$

Section-II – Answer All Questions (2 Marks Each)


- Q9.** If the current as shown in the waveform below, is passed through $2\ \Omega$ resistor, [2M]
the average power absorbed (over one cycle) by the resistor is ____?

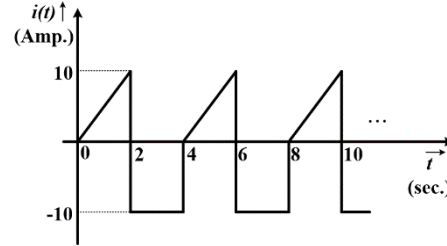- a) 0 W
b) 12.5 W
c) 16.3 W
d) 50 W
e) 133.3 W




- Q10.** For the following network (N), the power absorbed by the load resistance $R_L = 6\ \Omega$ is 24 W. If the R_L is changed to $16\ \Omega$ then the power absorbed is 16 W. The value of Norton equivalent current (I_N) and Norton resistance (R_N) are: [2M]

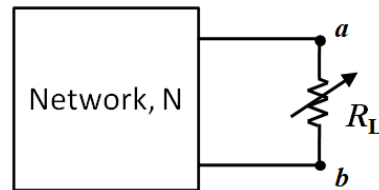- a) 5 A and $2\ \Omega$.
b) 5 A and $4\ \Omega$.
c) 10 A and $4\ \Omega$.
d) 10 A and $2\ \Omega$.




- Q11.** For the following network, the Thevenin's equivalent resistance and the Thevenin's equivalent voltage seen from the a-b terminals are, [2M]

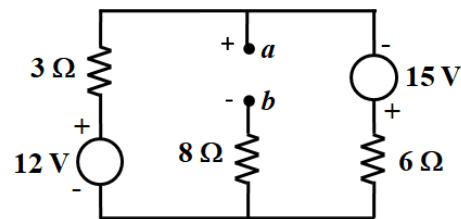- a) 12 V, $1.6\ \Omega$
b) 3 V, $10\ \Omega$
c) 27 V, $6.42\ \Omega$
d) -3 V, $17\ \Omega$



- Q12.** For the following circuit, the power delivered to the load (R_L), connected across a-b terminals, under the maximum power transfer condition is: [2M]

- a) 2.4 W** b) 4 W
c) 8 W d) 12 W

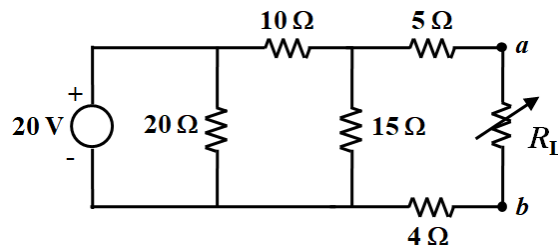

- Q13.** In a series RLC circuit, $R = 2\ \Omega$, $L = 1\ \text{mH}$, and $C = 0.4\ \mu\text{F}$. The half-power frequencies are ____? (Choose the closest values) [2M]

- a) 48 krad/s & 52 krad/s b) 48.5 krad/s & 51.5 krad/s
c) 48 krad/s & 50 krad/s **d) 49 krad/s & 51 krad/s**

- Q14.** For the circuit shown below, the magnitude of Thevenin's equivalent voltage, and Thevenin's equivalent impedance, between the load terminals a-b, are: [2M]

- a) 37.95 V, $6.48 + j2.64\ \Omega$
b) 37.95 V, $6.48 - j2.64\ \Omega$
c) 47.95 V, $6.48 + j2.64\ \Omega$
d) 47.95 V, $6.48 - j2.64\ \Omega$

