

Instructions: Attempt all the questions in sequence as they are written.
(The right-side numbers indicate marks.)

- Q1. (a) Show the Transfer Characteristics (V_o vs V_{in}) of a parallel negative clipping circuit by pn junction diode and clearly marking the on and off conditions of the non-ideal diode [5]
(b) Sketch i_R (current through $10\text{ k}\Omega$ resistor) and V_o (output voltage) for the network shown in Fig.1 below. The input signal V_i is a triangular waveform with 10 V as its peak value. The Si diodes used have 0.7 V as the forward bias voltage (cut-in voltage). [10]

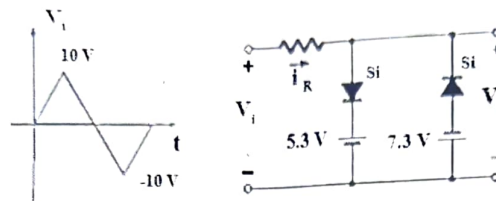


Fig.1

- Q2. Obtain the output voltage v_o for the rightmost $4.4\text{ k}\Omega$ resistor in the circuit shown in Fig.2 below. The input voltage v_i is a sinusoid with 100 V as its peak amplitude. The diodes are considered to be ideal. [10]

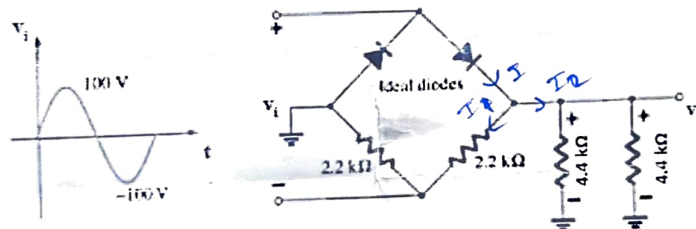


Fig.2

- Q3. (a) I_{CBO} and I_{CEO} . How are they different? How are they related? Are they typically close in magnitude? [5]
(b) The current gain of the transistor is $\beta = 120$. Determine I_C and V_{CE} for the circuit given in the Fig.3. [5]
(c) For the circuit in Fig.4 in which $|V_{BE}| = 0.7\text{ V}$ and $\beta = 20$, find the collector, base and emitter voltages and currents. [5]
- Q4. (a) Draw the basic construction of a p-channel JFET. Draw the circuit to show the proper biasing of the JFET and sketch the depletion region. [5]
(b) For the circuit in Fig.5, the transistor parameters are $I_{DSS} = 4\text{ mA}$ and $V_p = -3\text{ V}$. Find R_D such that $V_{DS} = |V_p|$. What is the value of I_D ? [5]

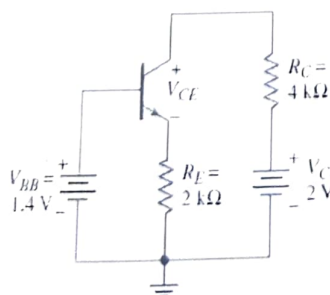


Fig.3

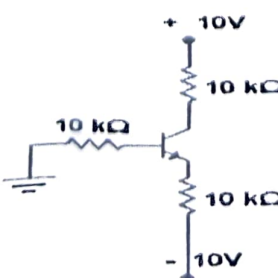


Fig.4

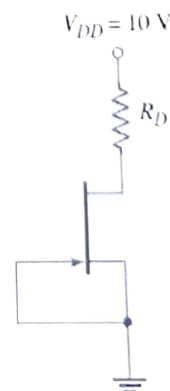


Fig.5

- Q5. (a) Describe in brief the important characteristics of an ideal op-amp which are necessary to understand the fundamental concepts of op-amp operation. [5]
 (b) Draw the schematic of a voltage follower using an ideal op-amp and derive its voltage gain. [5]
 Mention one important characteristic of a voltage follower.
- Q6. (a) In the differential amplifier shown in Fig.6, $R_1 = 10\text{ K}\Omega$, $R_2 = 10\text{ K}\Omega$, $R_3 = 100\text{ K}\Omega$, and $R_f = 100\text{ K}\Omega$. Determine the output voltage V_o if [5]
 (i) $V_1 = 5\text{ mV}$ and $V_2 = 0\text{ mV}$, (ii) $V_1 = 0\text{ mV}$ and $V_2 = 5\text{ mV}$, (iii) $V_1 = 50\text{ mV}$ and $V_2 = 25\text{ mV}$, (iv) $V_1 = 25\text{ mV}$ and $V_2 = 50\text{ mV}$ [5]
 (b) Find v_o and i_o in the op-amp circuit shown in Fig.7. [5]
 (c) If $v_1(t) = 20 \cos(3t)\text{ mV}$ and $v_2(t) = 2t\text{ mV}$ in Fig.8, find $v_o(t)$ for $t > 0$. Assume that the voltage across the capacitor is zero at $t = 0$. [5]

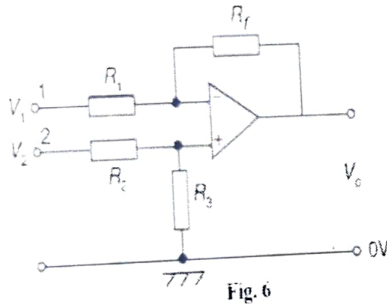


Fig. 6

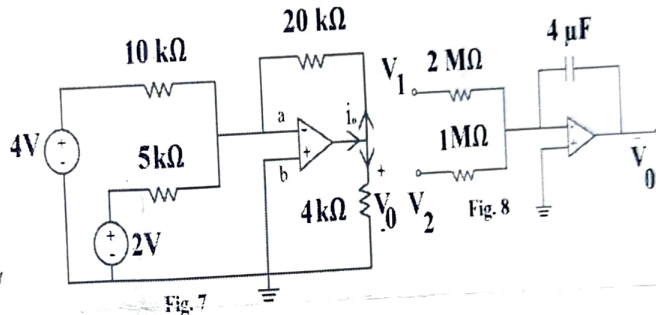


Fig. 7


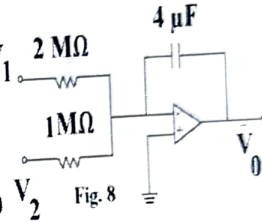


Fig. 8

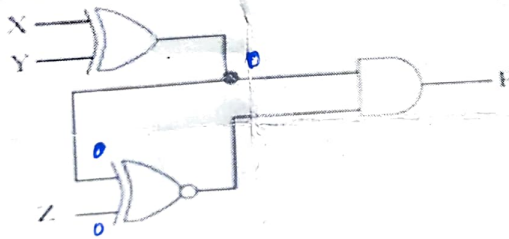- Q7. (a) Express output F in canonical SOP form? [2]



- (b) Convert $(57)_8$ into a number system whose radix is 6. [2]
 (c) Convert $(46)_{10}$ into octal system. [2]
 (d) Perform $(-7)_{10} - (13)_{10}$ in binary using 1's complement method. [4]
 (e) Simplify $F = \overline{(A + BC)} (\overline{AB} + ABC)$ [5]
 Q8. (a) Prove the following using Boolean algebraic theorem [5]
 $\overline{ABC} + \overline{A}BC + A\overline{B}C + ABC = AB + BC + CA$
 (b) Consider the Boolean function $f(A,B,C,D) = \sum m(1,3,7,11,15) + \sum d(0,2,5)$ where m stands for min-term and d stands for don't care. [5]
 Simplify the above function using K-Map and implement the simplified function using minimum number of 2-input NAND gates only.